

# **The Effect of Correlated Level Shifting on Noise Performance in Switched Capacitor Circuits**

Benjamin Hershberg, Tawfiq Musah,  
Skyler Weaver, Un-Ku Moon

(Presented by Taehwan Oh)

School of Electrical Engineering and Computer Science  
Oregon State University


# Presentation Outline

---

- Background
  - CLS (Correlated Level-Shifting)
  - Split-CLS
- Theoretical Noise Analysis
- Numerical and Simulation Results
- Conclusion

# Background


# Correlated Level Shifting (CLS)

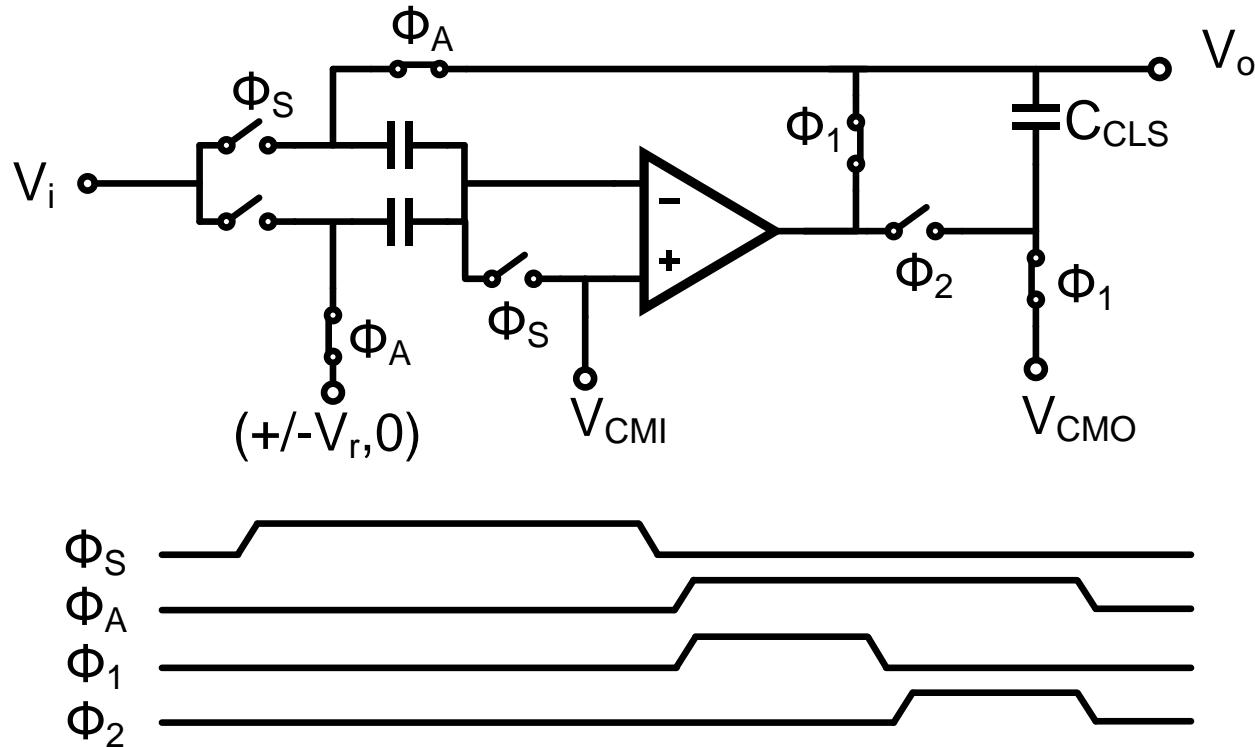

- Finite opamp gain error becomes  $1/A^2$
- Opamp output tied to different nodes in  $\Phi_1$  and  $\Phi_2$

[Gregoire, JSSC 2008]

# CLS Basic Operation

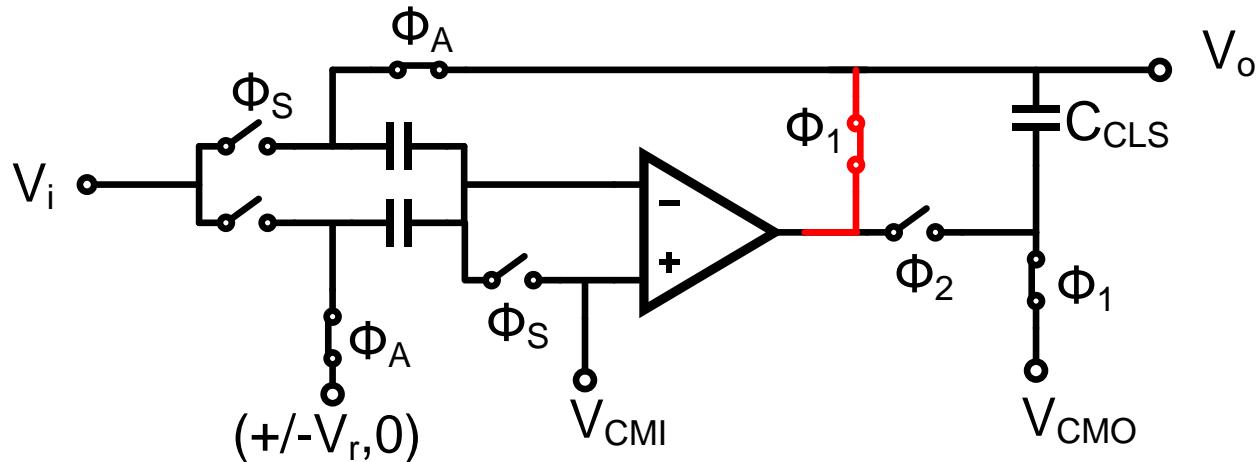


$\Phi_1$  :

- opamp charges output directly
- processes full signal

**Opamp Design Requirements**

	$\Phi_1$	$\Phi_2$
<b>Output Swing</b>	Large	Small
<b>Slew Rate</b>	Large	Small

# CLS Basic Operation

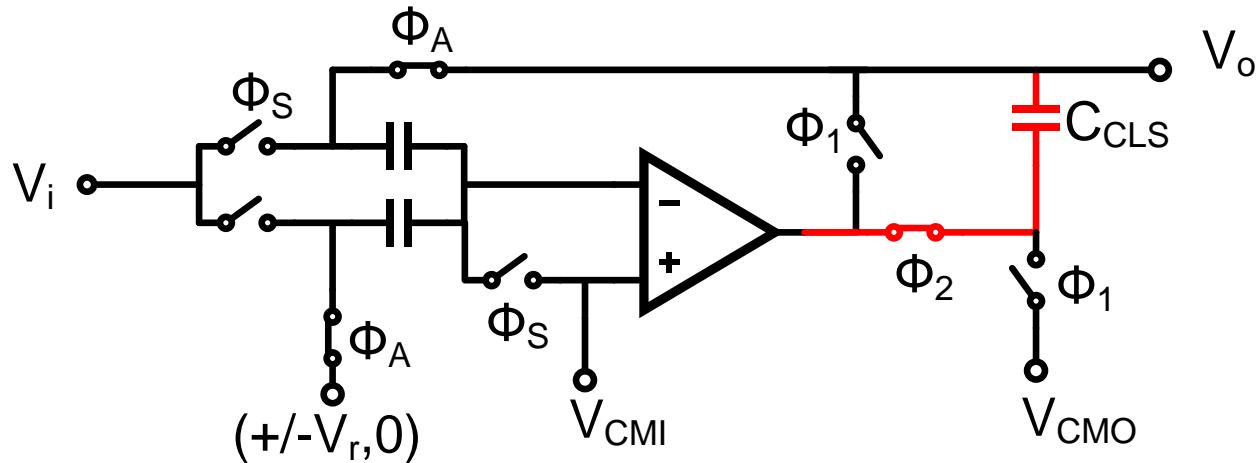

$\Phi_2$ :

- opamp is level shifted to mid-rail
- processes error only

## Opamp Design Requirements

	$\Phi_1$	$\Phi_2$
Output Swing	Large	Small
Slew Rate	Large	Small

# Observation: Split-CLS


---

- Use separate charging devices for  $\Phi_1$  and  $\Phi_2$
- Optimized design for each phase
  - Increase overall accuracy & efficiency

## Opamp Design Requirements


	$\Phi_1$	$\Phi_2$
<b>Output Swing</b>	Large	Small
<b>Slew Rate</b>	Large	Small

# Split-CLS (Correlated Level Shifting)

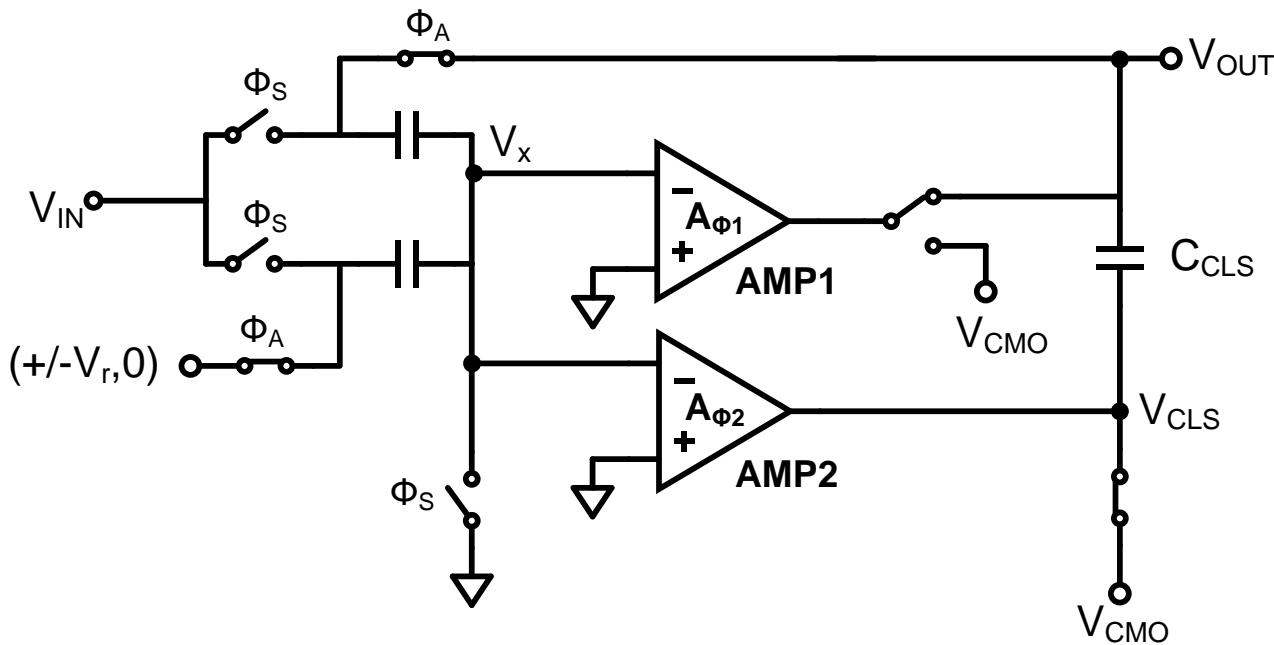

- Split-CLS
  - Generalized form of Correlated Level Shifting (CLS)
  - Finite opamp gain error approx.  $1 / (A_1 * A_2)$

# Split-CLS (Correlated Level Shifting)

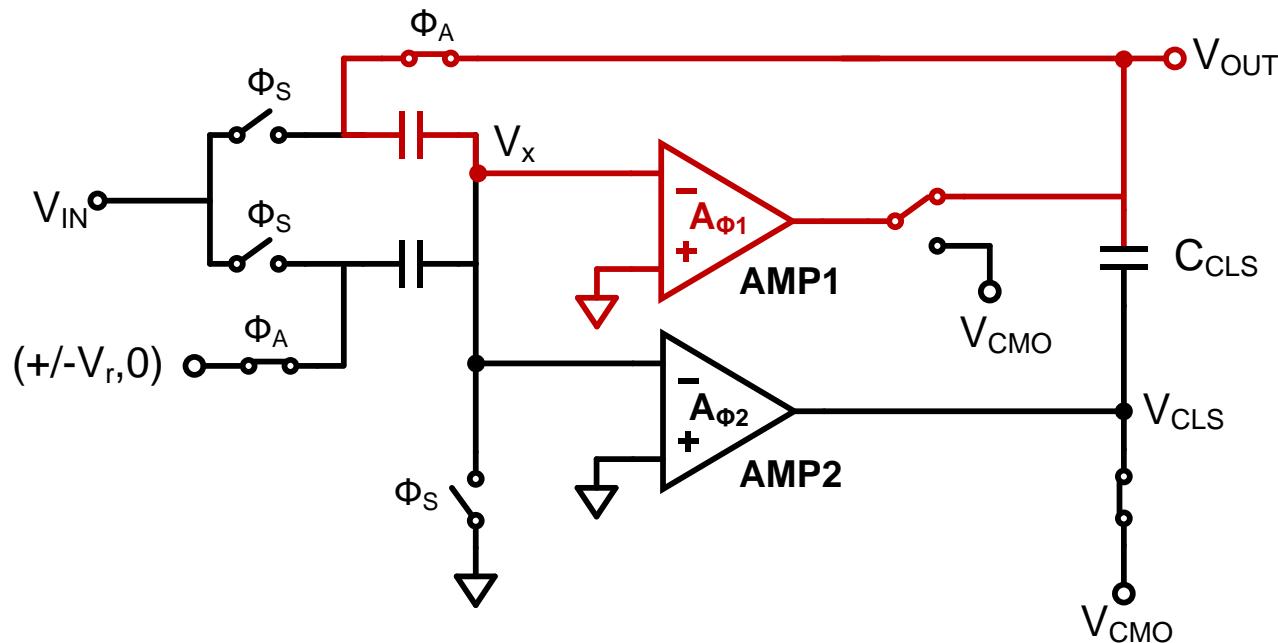


$\Phi_1$ :

- amp charges output directly
- processes full signal

**Amplifier Design Requirements**

	$\Phi_1$	$\Phi_2$
<b>Output Swing</b>	<b>Large</b>	<b>Small</b>
<b>Slew Rate</b>	<b>Large</b>	<b>Small</b>

# Split-CLS (Correlated Level Shifting)

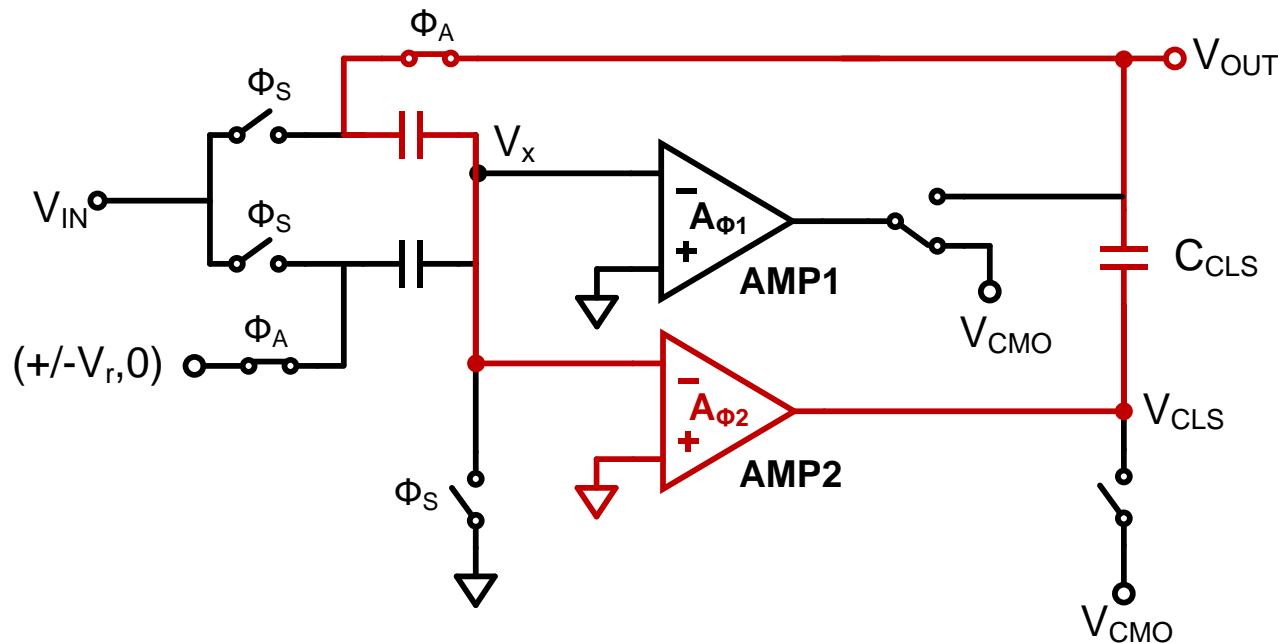


$\Phi_2$ :

- opamp is level-shifted to mid-rail
- processes error only

Amplifier Design Requirements


	$\Phi_1$	$\Phi_2$
Output Swing	Large	Small
Slew Rate	Large	Small

# Split-CLS (Correlated Level Shifting)

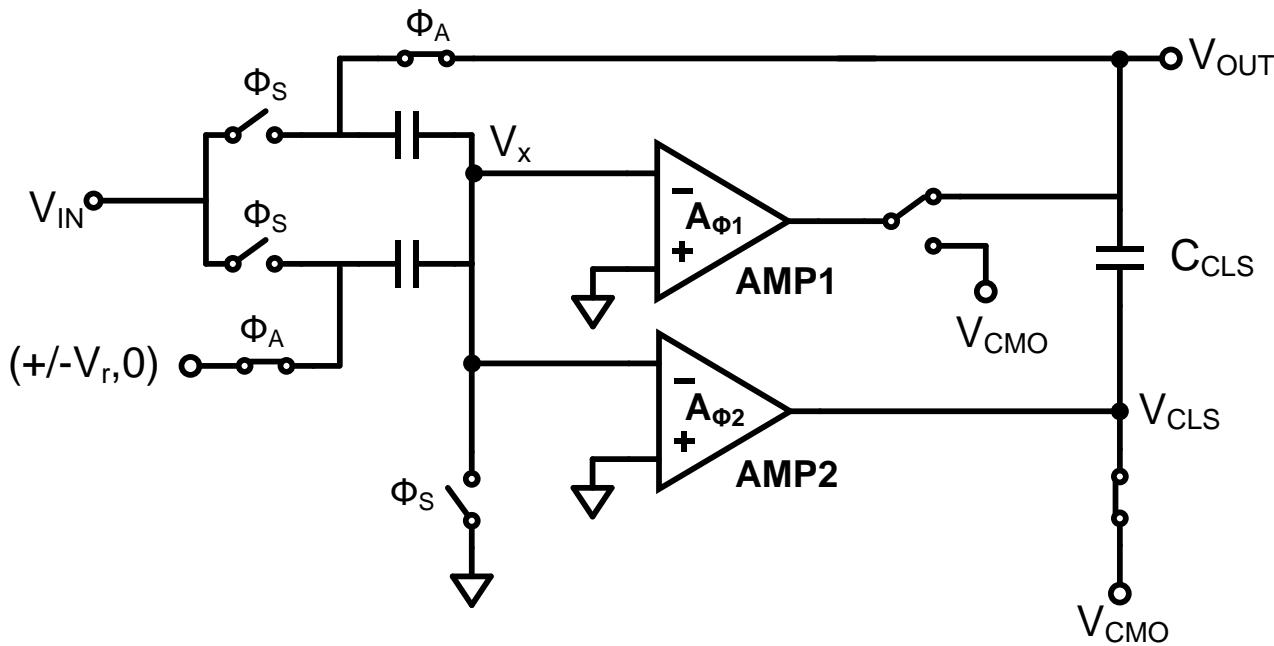


- Many options for coarse amp / fine amp...
  - ISSCC 2010: ZCBC (coarse) + Telescopic opamp (fine)
  - ISSCC 2012: Ring Amplifier (coarse) + Telescopic opamp (fine)

# Split-CLS: ISSCC 2010

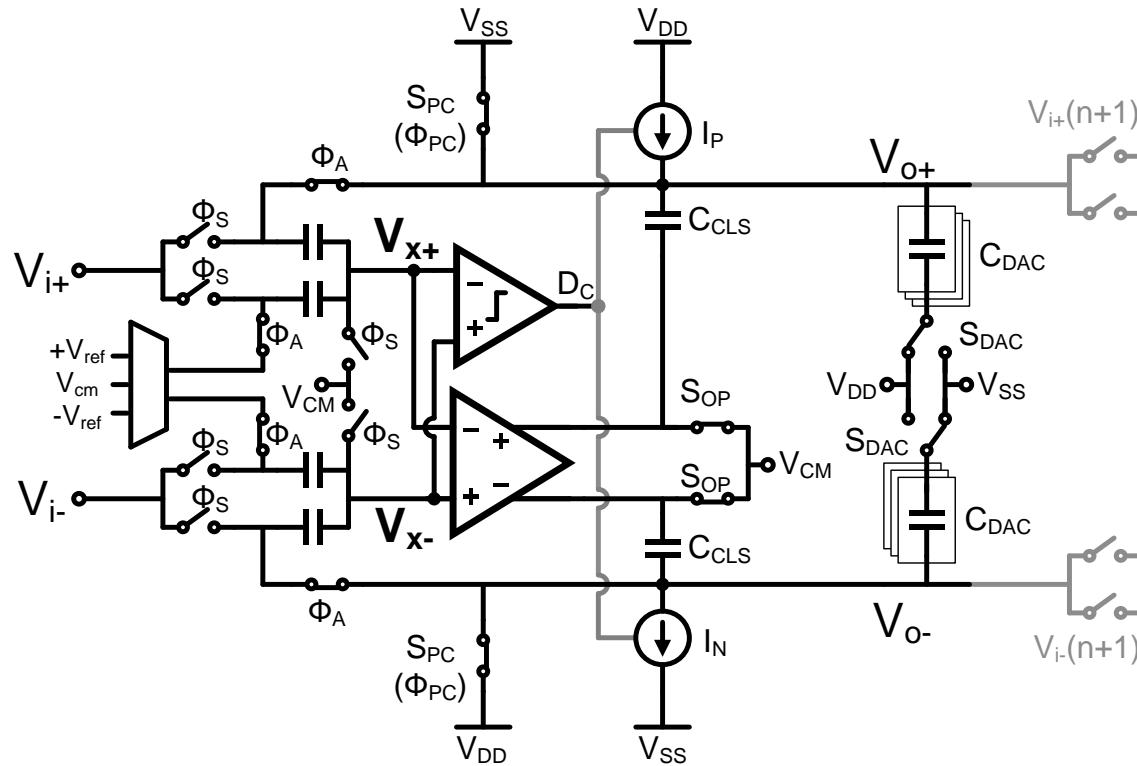

- Coarse Amp: Zero-crossing based circuit (ZCBC)
- Fine Amp: Double-cascoded telescopic opamp

# Split-CLS: ISSCC 2012

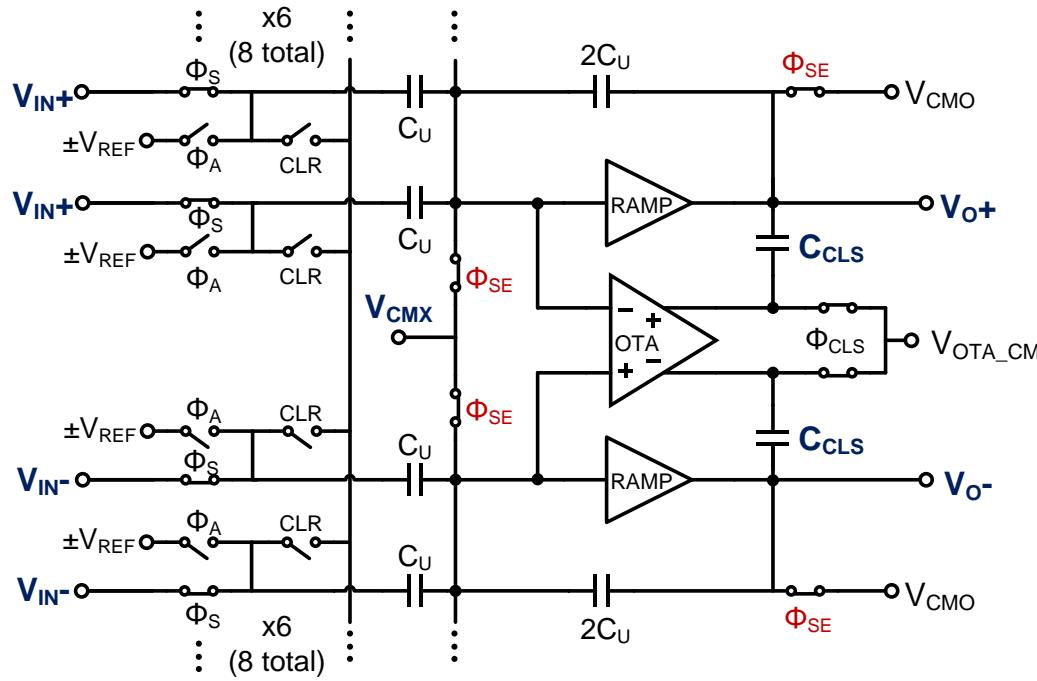

- Coarse Amp: Pseudo-differential Ring Amplifier (ringamp)
- Fine Amp: Double-cascoded telescopic opamp
- Best FoM of any high-resolution ADC ever reported
  - 76.8dB SNDR, 95.4dB SFDR, 5.1mW, 20Msps, 45fJ/c-step FoM

# Noise Analysis


# Noise Analysis: Split-CLS

---


- The size of  $C_{CLS}$  affects:
  - Accuracy - feedback factor
  - Speed - total load capacitance seen by fine amp
  - Opamp requirements - fine amp output swing requirement
- How does level-shifting affect noise performance
  - Help? Hurt?
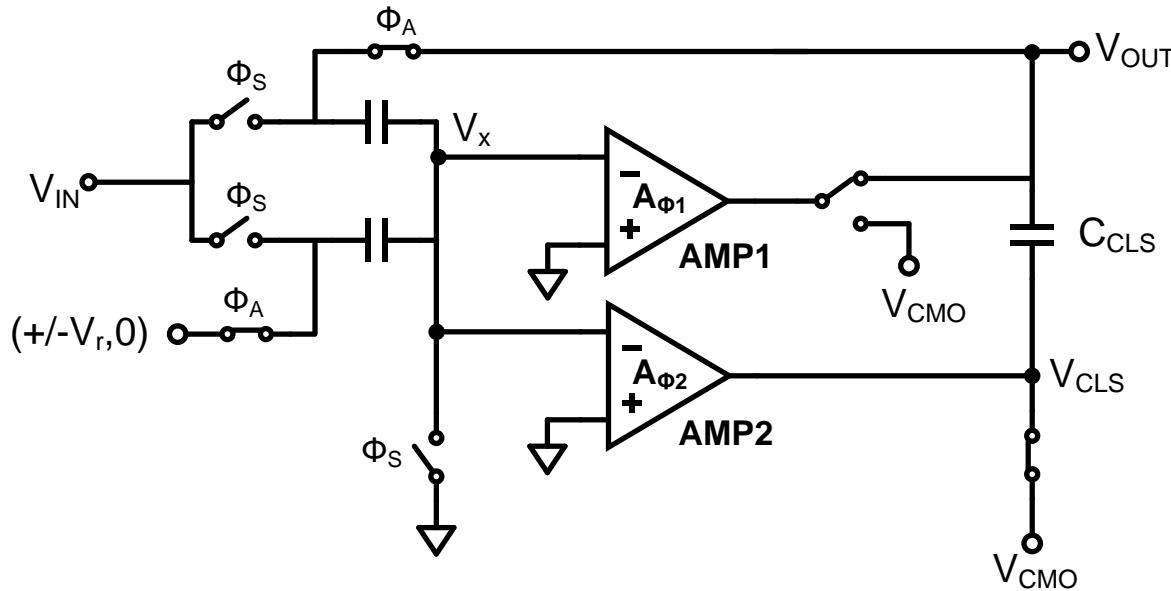
# Noise Analysis: Split-CLS


- Noise due to AMP1 is suppressed by gain of AMP2
  - Final noise determined by AMP2
- Only fine phase configuration must be considered



# Noise Analysis: Split-CLS

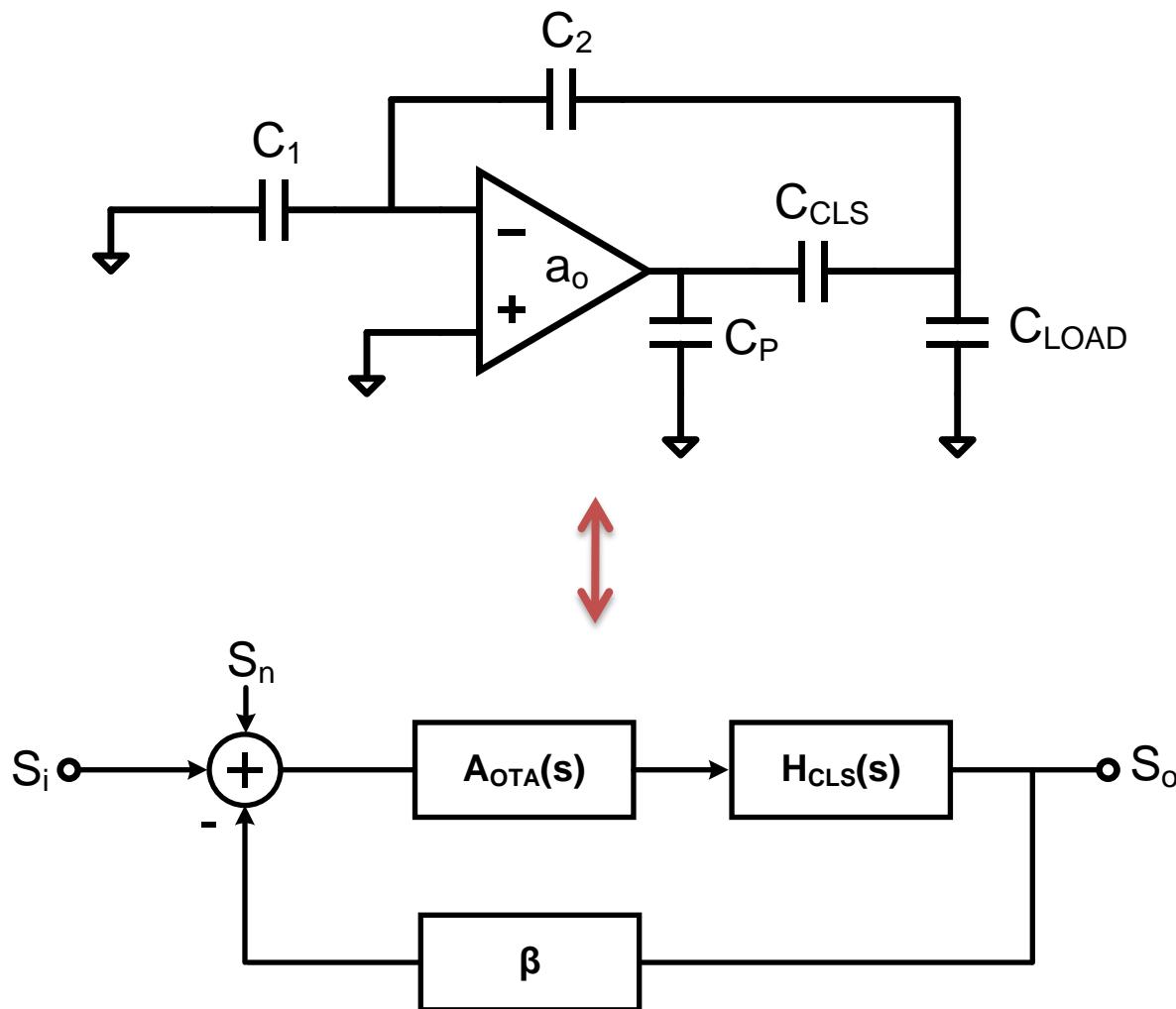


# Noise Analysis: Split-CLS

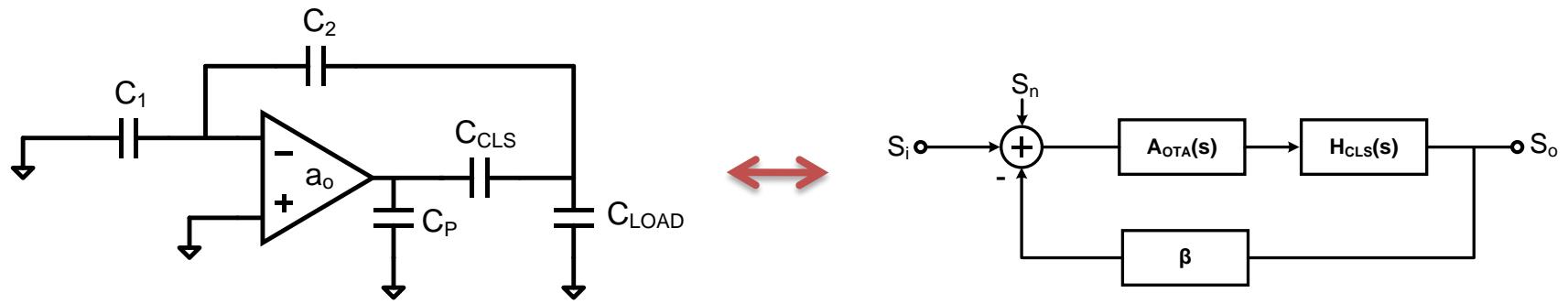

$$C_{LOAD} = \alpha(C_1 + C_2) \quad (1)$$

$$\beta = \frac{C_2}{C_1 + C_2}. \quad (2)$$


# Noise Analysis: Split-CLS

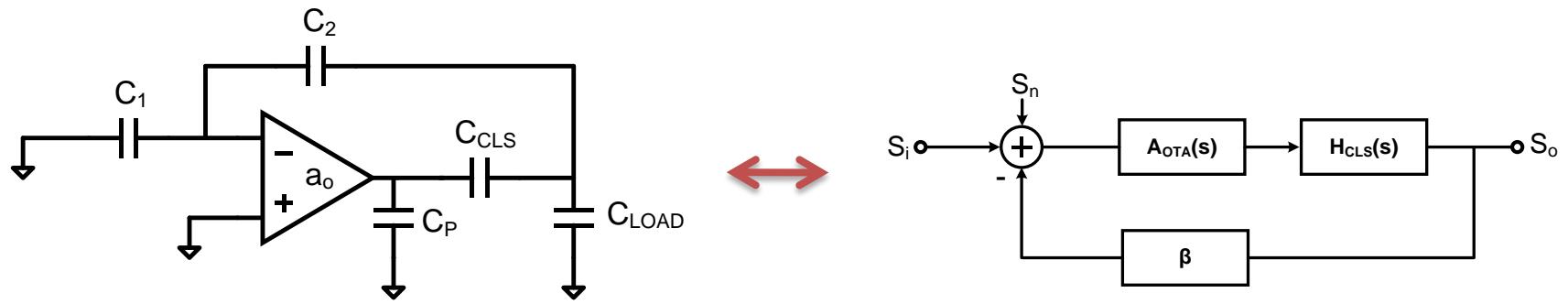

$$H_{\text{CLS}}(s) = \frac{C_{\text{CLS}}}{C_{\text{CLS}} + C_{\text{LD}}} \quad (3)$$

$$C_{\text{LD}} = C_{\text{LOAD}} + \frac{C_1 \cdot C_2}{C_1 + C_2}. \quad (4)$$

# Noise Analysis: Split-CLS

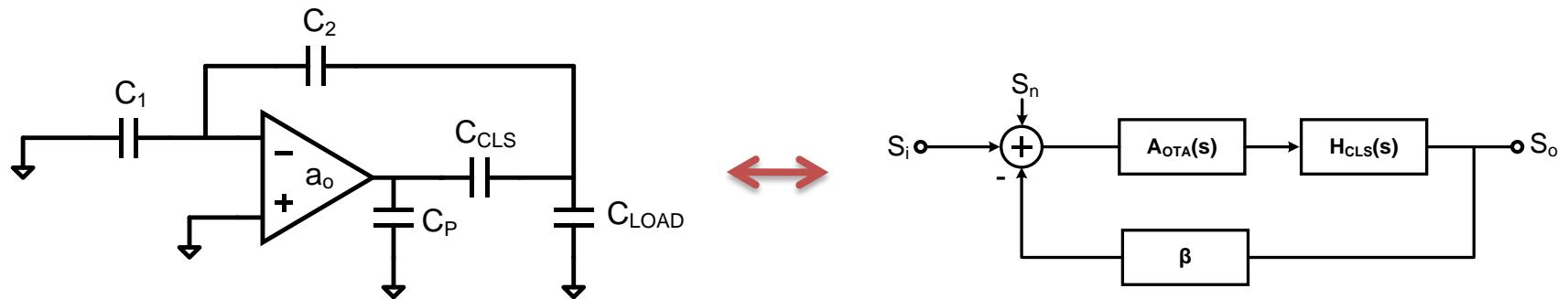


Single-stage opamp (as is commonly used in Split-CLS) has one dominant pole:

$$C_{OTA} = C_P + \frac{C_{CLS} \cdot C_{LD}}{C_{CLS} + C_{LD}} \quad (5)$$

$$A_{OTA}(s) = \frac{a_o}{1 + \frac{s}{p_1}} \Big|_{p_1 = \frac{1}{R_O C_{OTA}}} \quad (6)$$



# Noise Analysis: Split-CLS

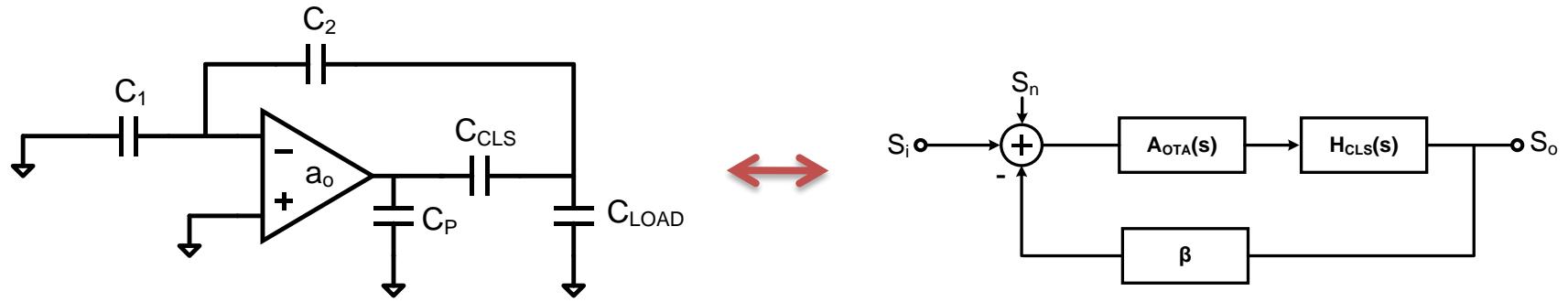


$$A_{fp}(s) = A_{\text{OTA}}(s) \cdot H_{\text{CLS}}(s) \quad (7)$$

$$H_n(s) = \frac{A_{\text{OTA}}(s) \cdot H_{\text{CLS}}(s)}{1 + \beta \cdot A_{\text{OTA}}(s) \cdot H_{\text{CLS}}(s)}. \quad (8)$$

# Noise Analysis: Split-CLS

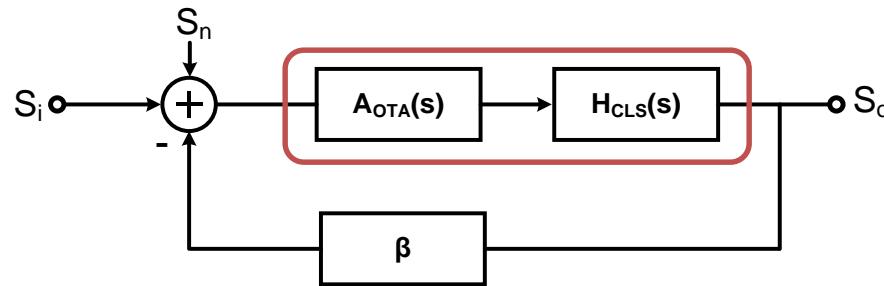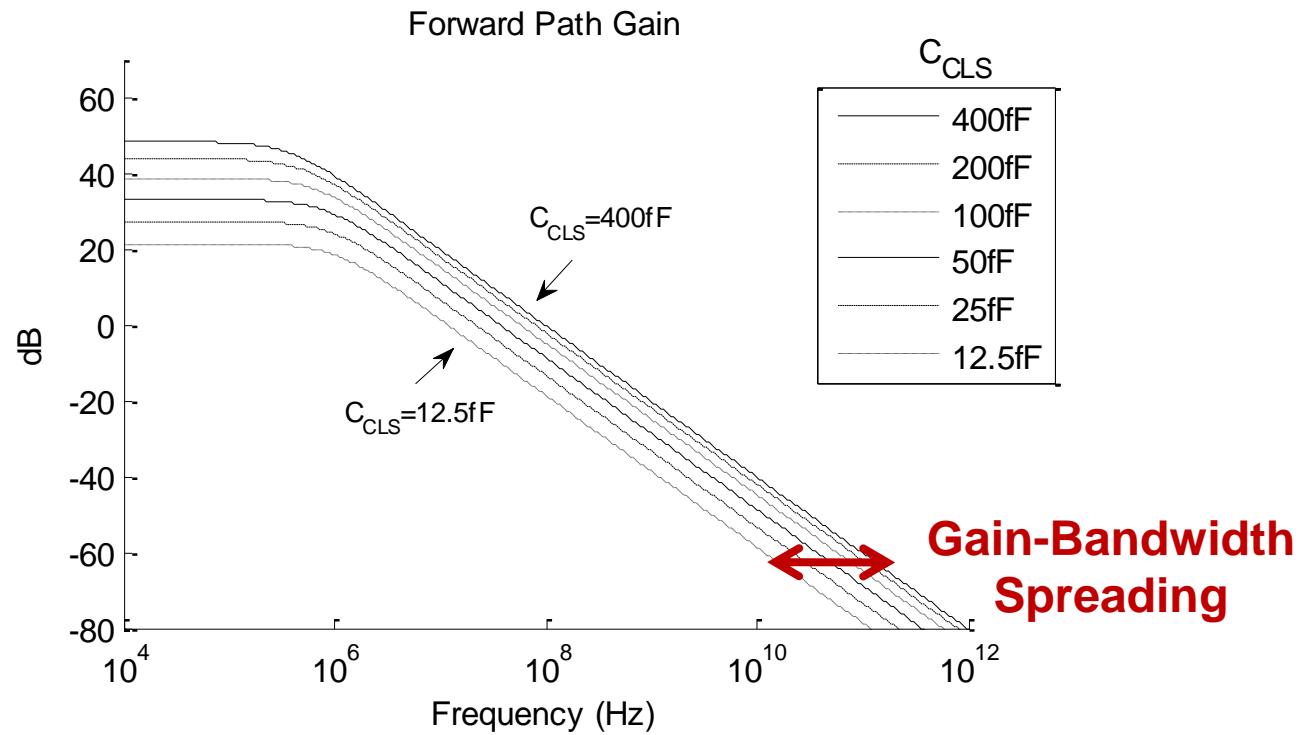

# Noise Analysis: Split-CLS

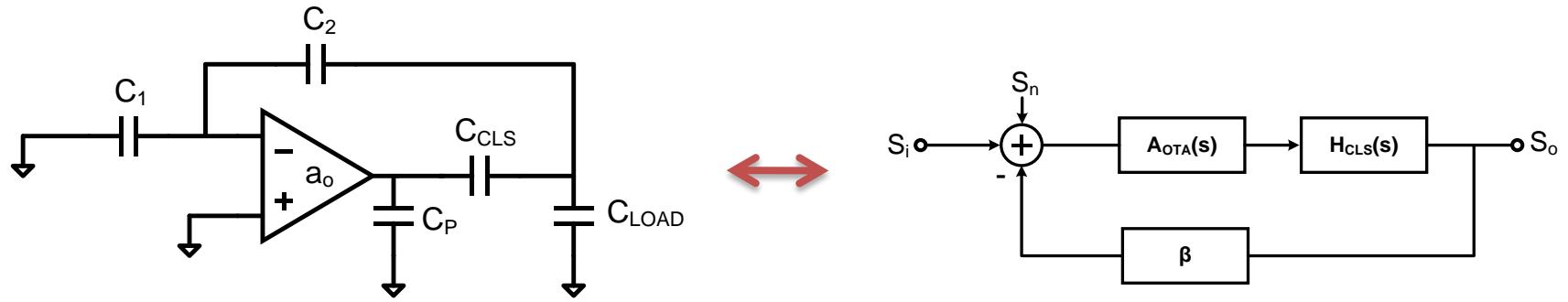


$$A_{fp}(s) = A_{OTA}(s) \cdot H_{CLS}(s)$$

$$C_{OTA} = C_P + \frac{C_{CLS} \cdot C_{LD}}{C_{CLS} + C_{LD}}$$

$$H_{CLS}(s) = \frac{C_{CLS}}{C_{CLS} + C_{LD}}$$

Normally, factors cancel & gain-bandwidth product is constant

# Noise Analysis: Split-CLS

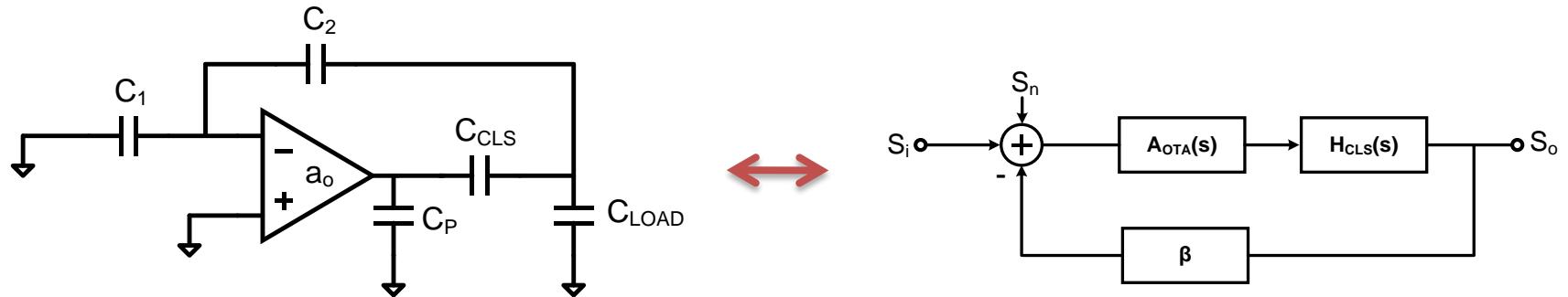



$$A_{fp}(s) = A_{OTA}(s) \cdot H_{CLS}(s)$$

$$C_{OTA} = C_P + \frac{C_{CLS} \cdot C_{LD}}{C_{CLS} + C_{LD}}$$


$$H_{CLS}(s) = \frac{C_{CLS}}{C_{CLS} + C_{LD}}$$

Presence of  $C_P$  causes gain-bandwidth spreading when  $C_{CLS}$  is varied

# Noise Analysis: Split-CLS

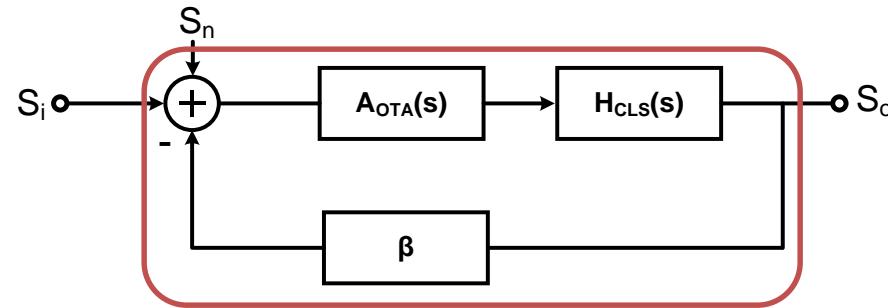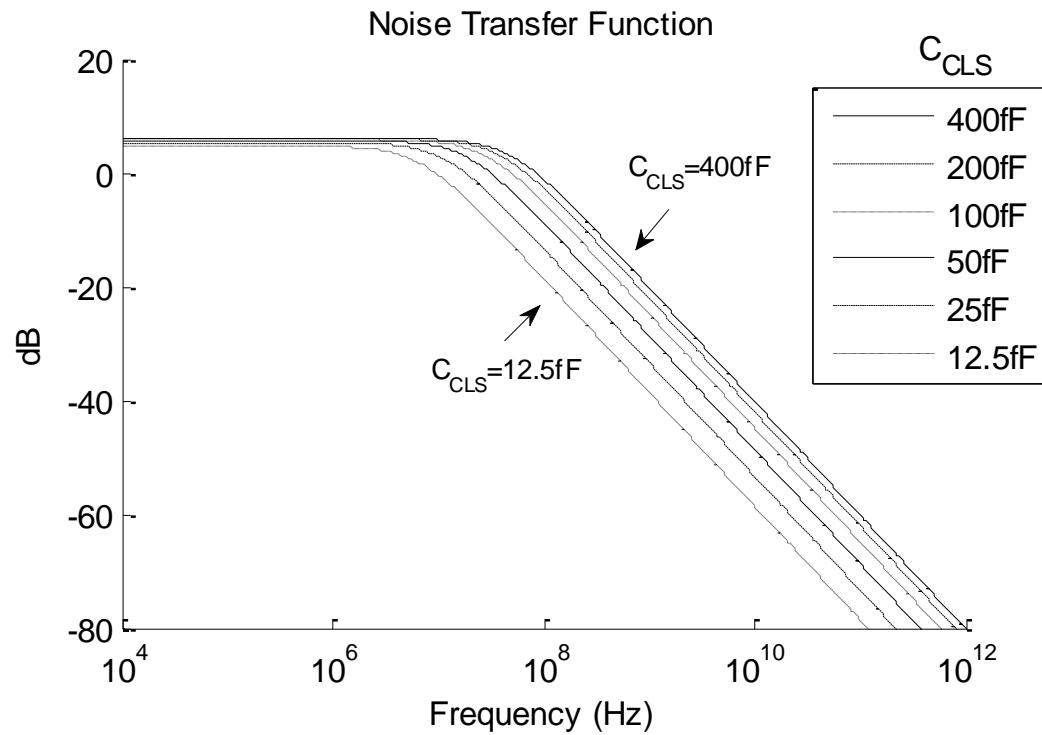


# Noise Analysis: Split-CLS

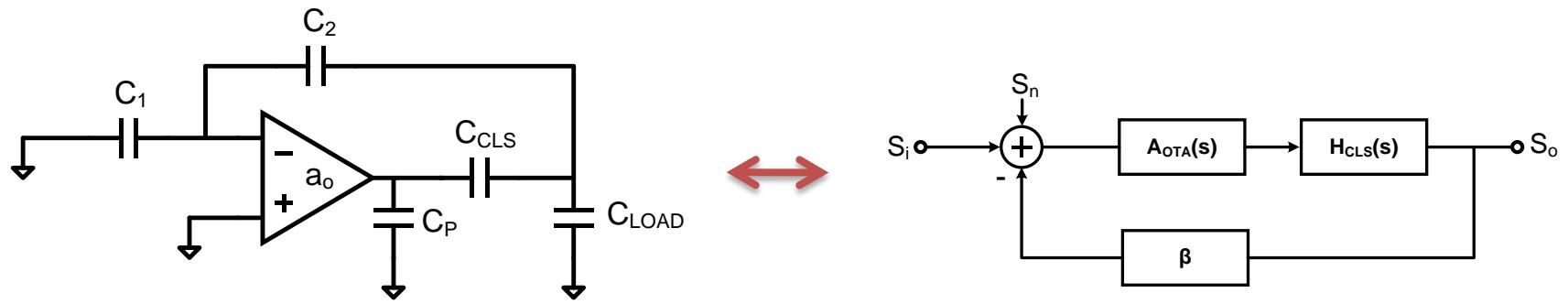

Total integrated noise power for noise source  $S_n(f)$ :


$$\tilde{v}_{no}^2 = \int_0^{\infty} S_n(f) \cdot |H_n(2\pi f)|^2 \, df. \quad (10)$$

# Noise Analysis: Split-CLS

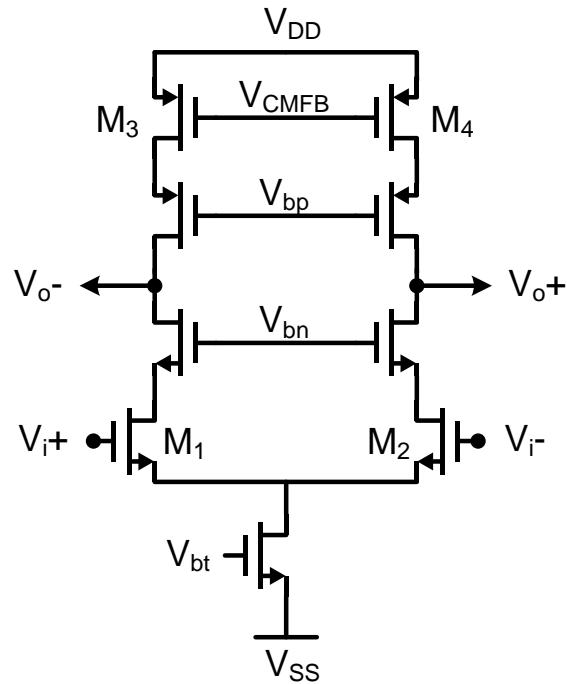

- Telescopic opamp used as noise source
- $M_1$ ,  $M_2$ ,  $M_3$ ,  $M_4$  are the dominant noise contributors
  - Can be modeled as single input-referred noise contributor



# Noise Analysis: Split-CLS

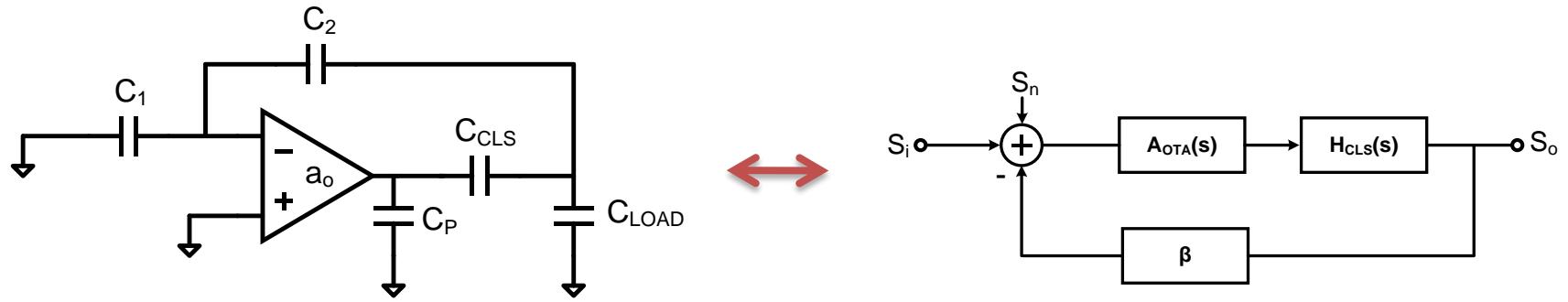


When 1/f noise is entirely in passband of  $A_{OTA}(s)$ , noise sources can be treated as frequency-independent constants:

$$\tilde{v}_{no}^2 = v_{n(1/f)}^2 + \int_0^{\infty} S_{n(white)} \cdot |H_n(2\pi f)|^2 \, df \quad (11)$$

# Noise Analysis: Split-CLS

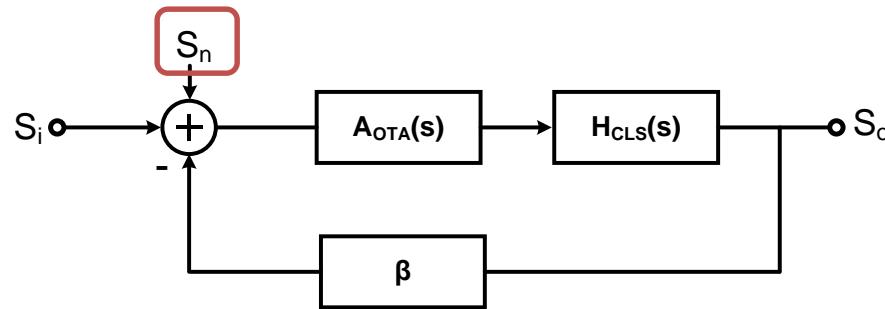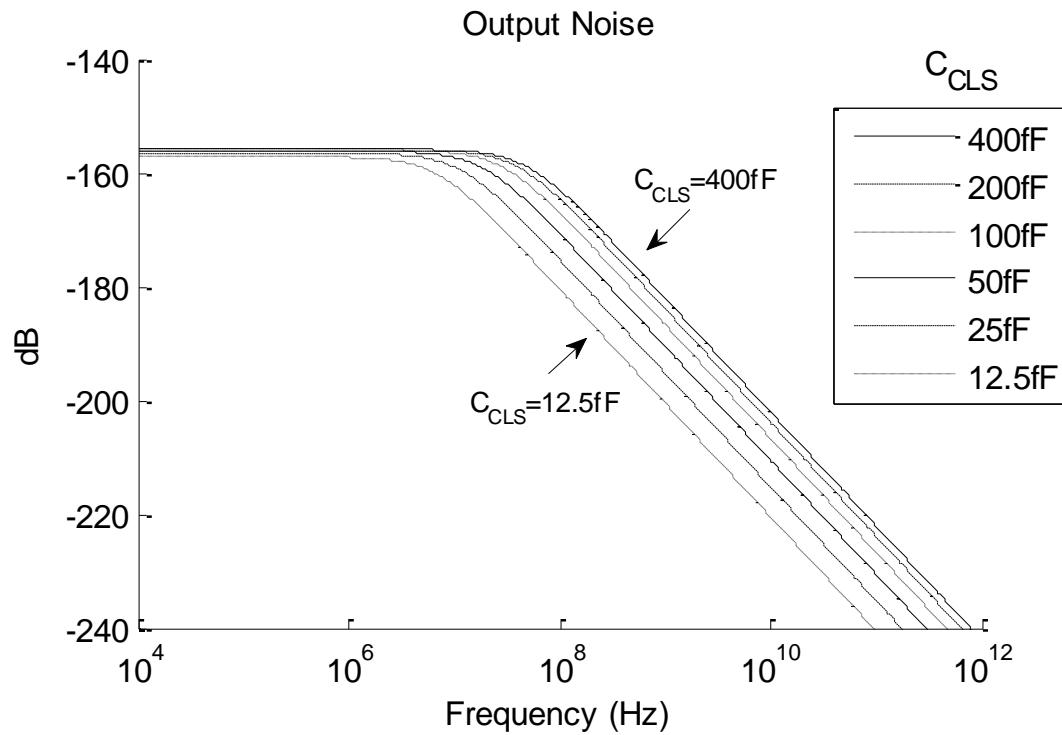

# Noise Analysis: Split-CLS

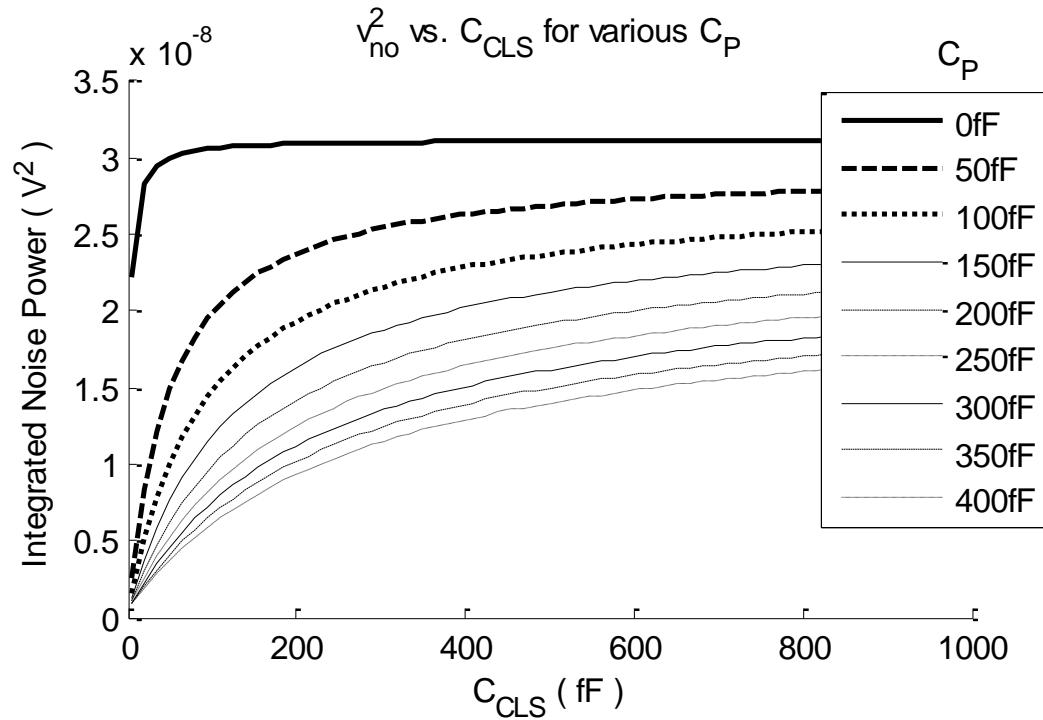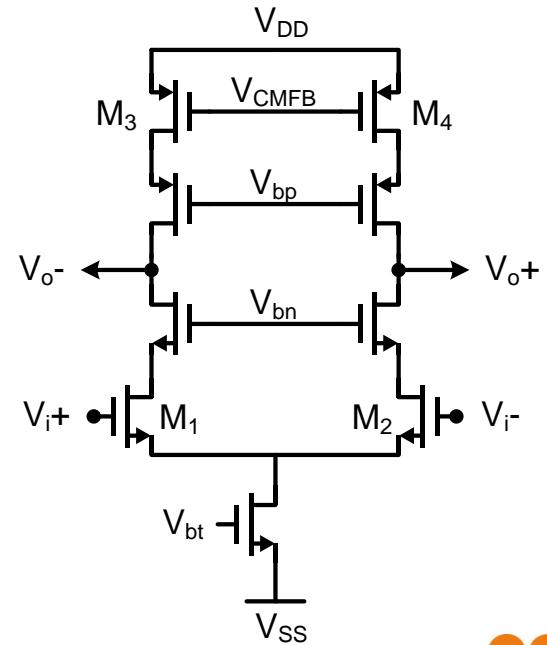
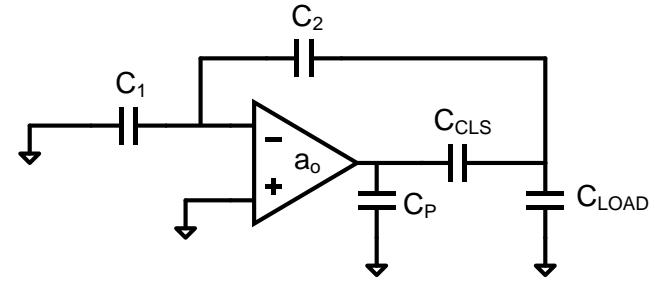

$$C_P \gg \frac{C_{CLS} \cdot C_{LD}}{C_{CLS} + C_{LD}} \rightarrow C_{CLS} \text{ and noise are heavily correlated.}$$
$$C_P \ll \frac{C_{CLS} \cdot C_{LD}}{C_{CLS} + C_{LD}} \rightarrow C_{CLS} \text{ and noise are weakly correlated.}$$

(Mostly likely case in practical designs.)




# Comparison with Simulation

# Comparison with Simulation

- Extracted values
  - $C_P = 45\text{fF}$
  - $a_o = 58.4\text{dB}$
  - $C_1 = C_2 = 400\text{fF}$
  - $C_{LOAD} = 640\text{fF}$
  - $V^2_{n(1/f)} = 6.31 \times 10^{-10} \text{ V}^2$
  - $S_{n(\text{white})} = 6.17 \times 10^{-17} \text{ V}^2/\text{Hz}$






# Comparison with Simulation

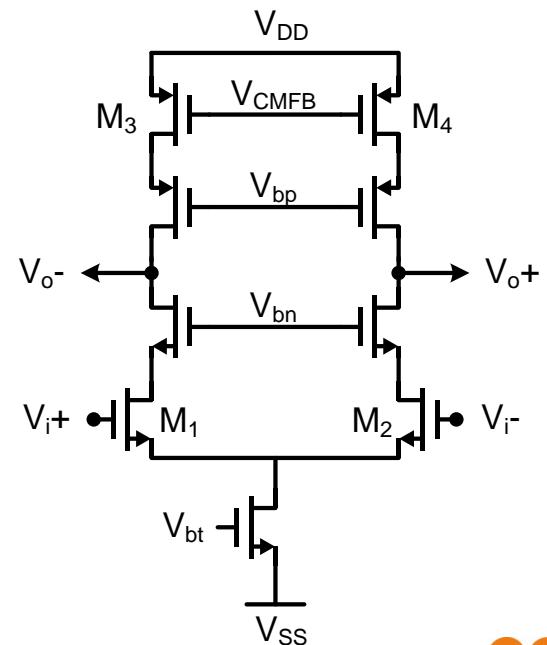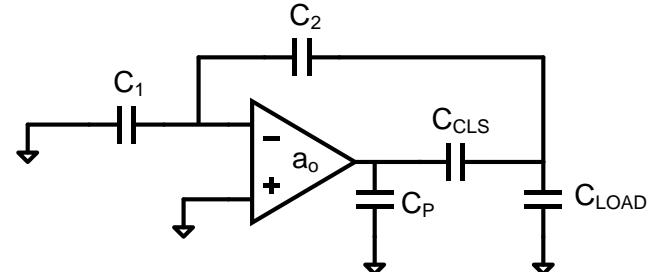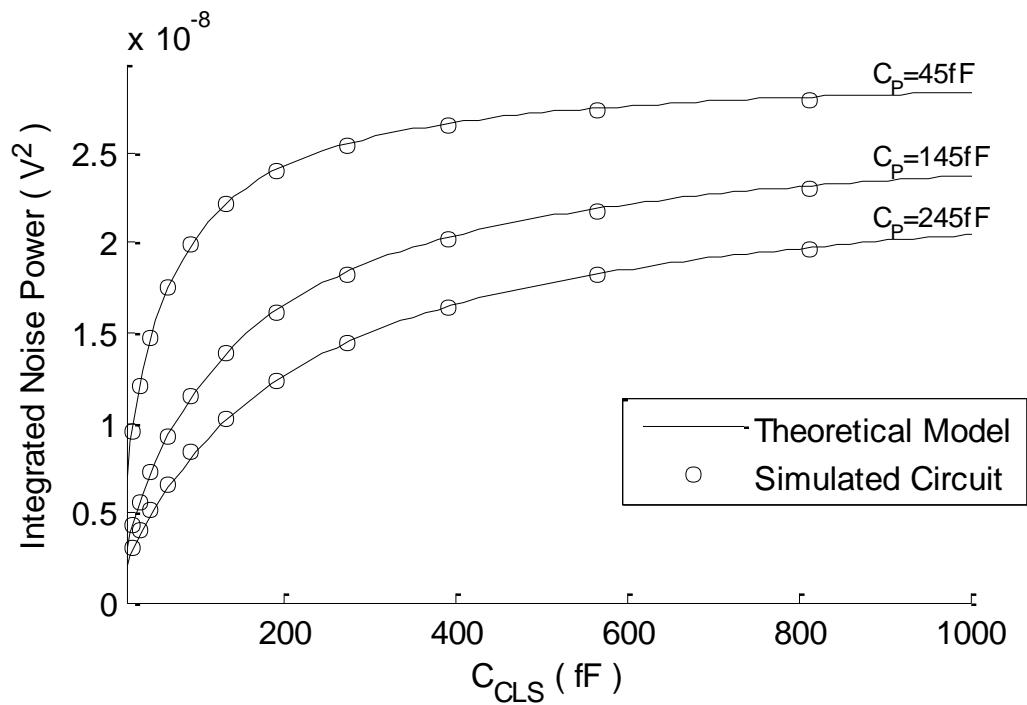

- Simulation and Theoretical model found to be in good agreement.

# Comparison with Simulation

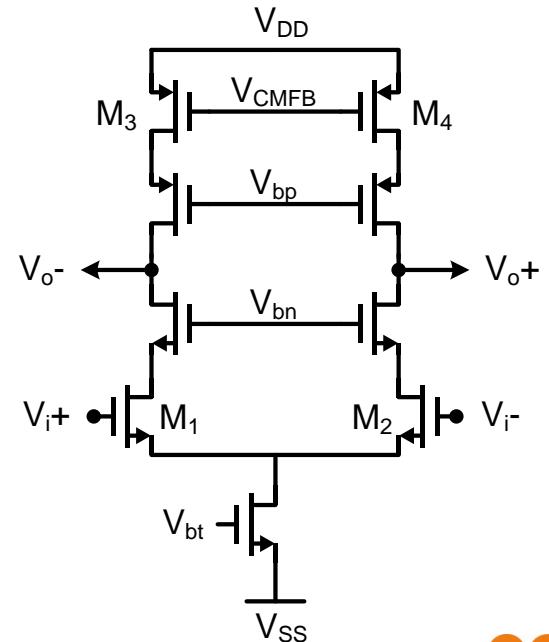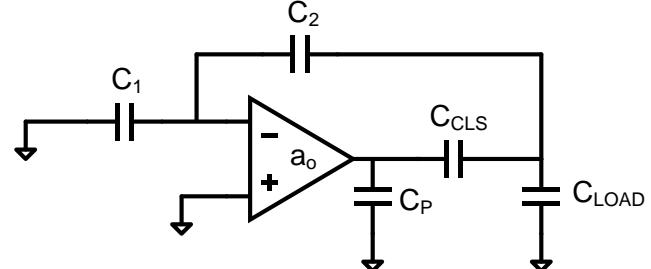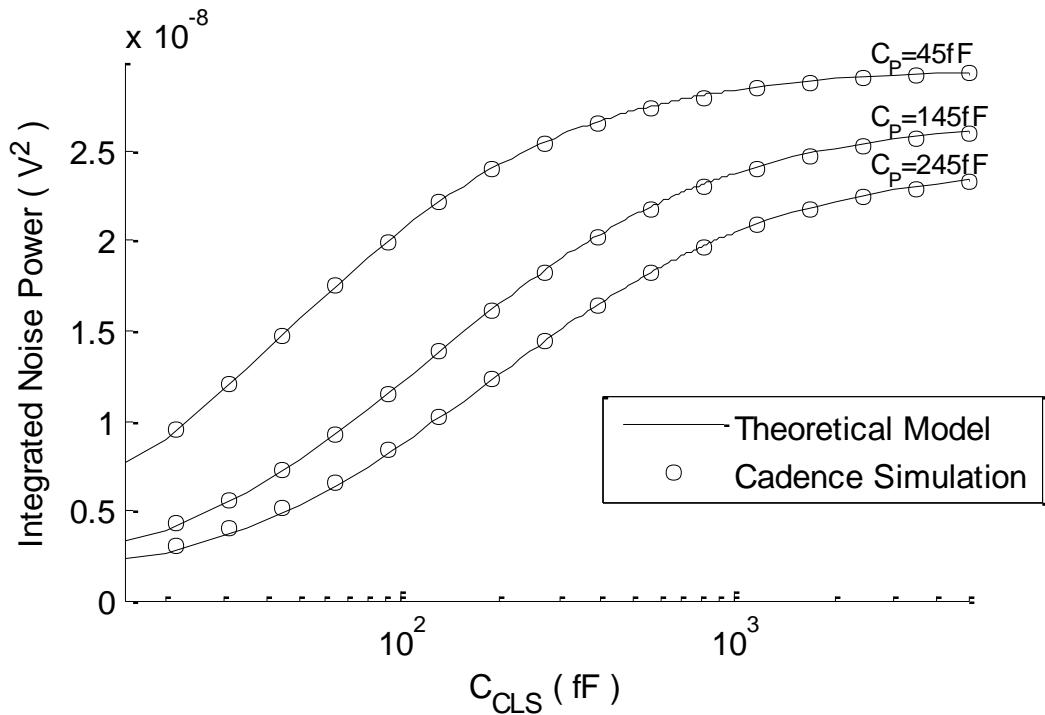

- Simulation and Theoretical model found to be in good agreement.

# Conclusion

# Conclusion

---

- CLS and Split-CLS reduce finite-opamp gain error by approximately  $1/A^2$
- Addition of  $C_{CLS}$  network to MDAC structure introduces bandwidth spreading dependent on  $C_{CLS} \leftrightarrow C_P$  relation.
- For most practical Split-CLS designs,  $C_{CLS} \gg C_P$ 
  - $C_{CLS}$  should be large enough to minimize swing requirement, maintain sufficient loop gain.
  - $C_P$  is only intrinsic parasitic capacitances of opamp
- In practical cases, total integrated opamp noise is not significantly affected by Split-CLS.

# Thank You For Your Attention