

A 61.5dB SNDR Pipelined ADC Using Simple Highly-Scalable Ring Amplifiers

Benjamin Hershberg¹, Skyler Weaver¹,
Kazuki Sobue², Seiji Takeuchi²,
Koichi Hamashita², Un-Ku Moon¹

¹Oregon State University, Corvallis, OR, USA

²Asahi Kasei Microdevices, Atsugi, Japan

An Incomplete Solution

- Goal: develop truly scalable amplifiers
 - Conventional opamps are fundamentally ill-suited for nanoscale CMOS
 - Efficiency in amplification-based designs is actually getting *worse*
- ADCs
 - Amplifier-less ADCs (i.e. SARs) provide excellent scalability for *some* of the design space
 - Scalable amplifiers are needed to cover the *entire* ADC design space
- The more scalable options we have, the better

Beating the Trend


A scalable amplifier must

- Operate well *in* nanoscale CMOS
- Improve *with* nanoscale CMOS

Circuit level requirements

- Minimize SNR loss from low-voltage, degrading r_o
- Exploit digital scaling benefits
- Avoid conventional RC-based settling

Beating the Trend

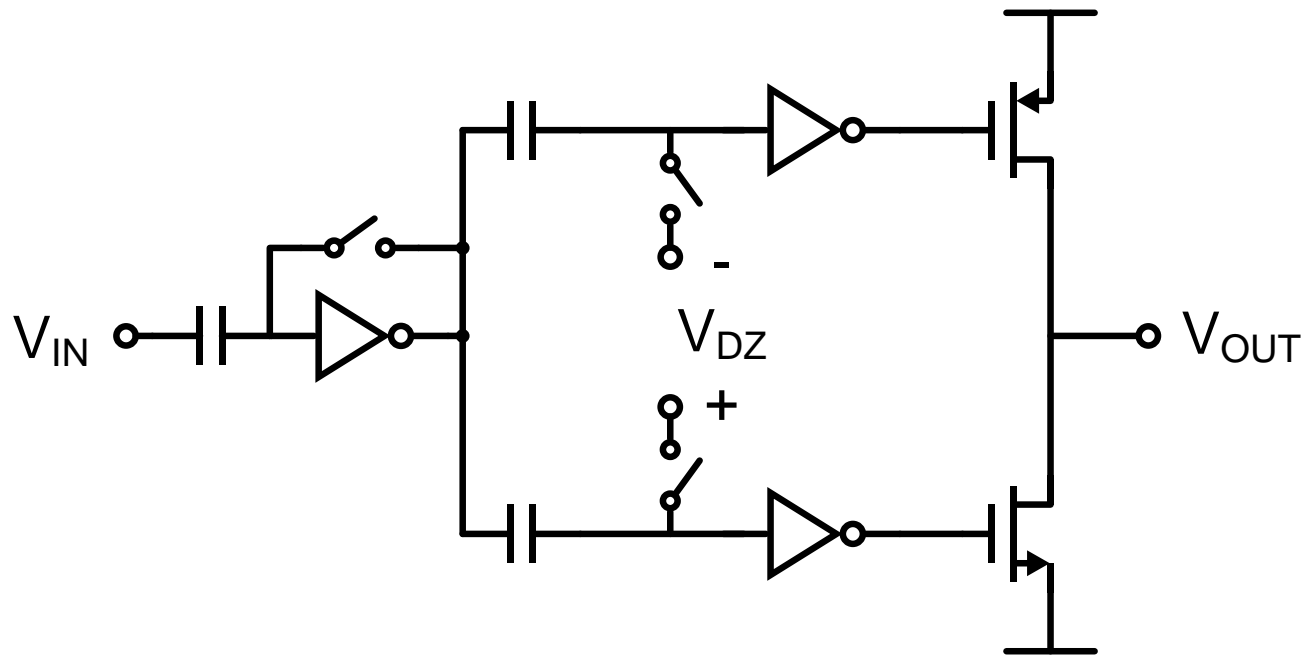


Ring Amplifier (Ringamp, RAMP)

Ring Amplification


Basic Theory

Ring Amplifier: Basic Theory

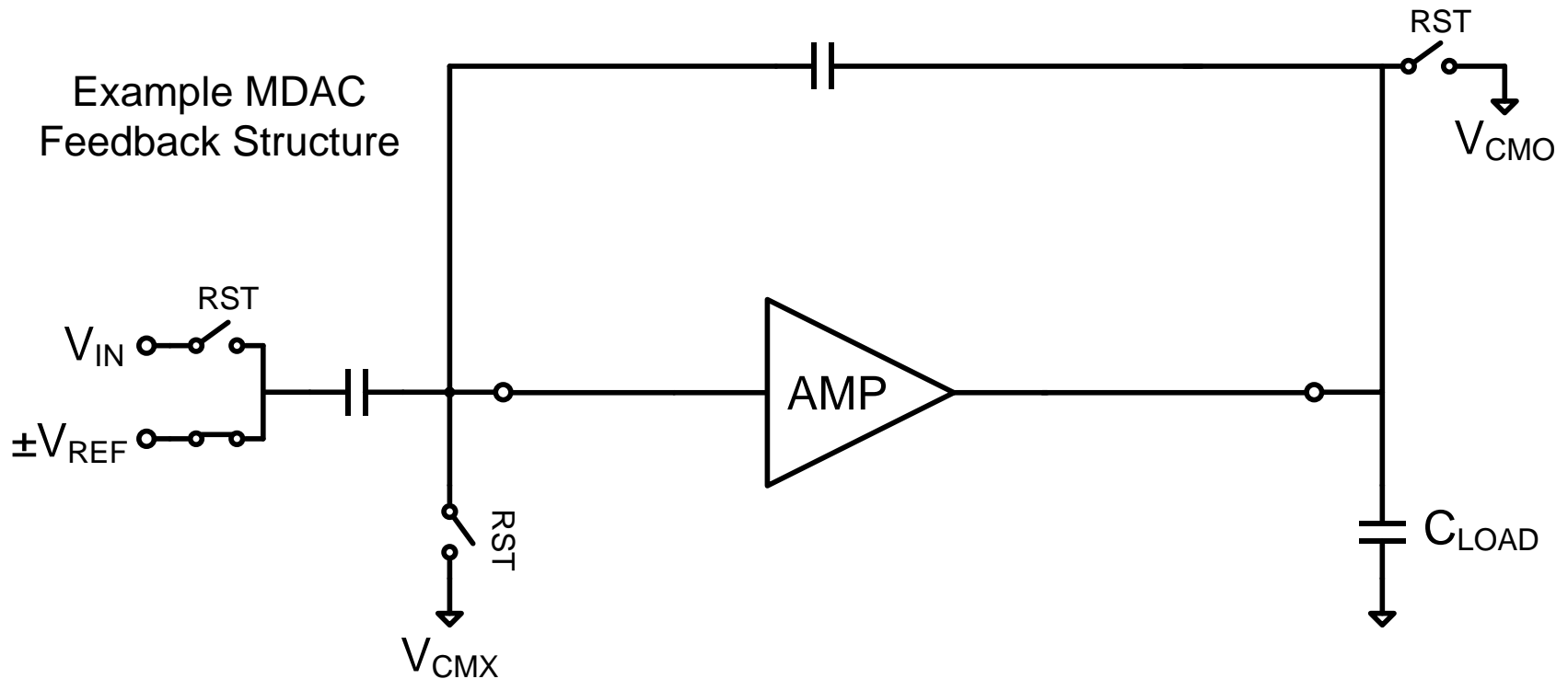


- Basic MDAC test structure

Ring Amplifier: Basic Theory

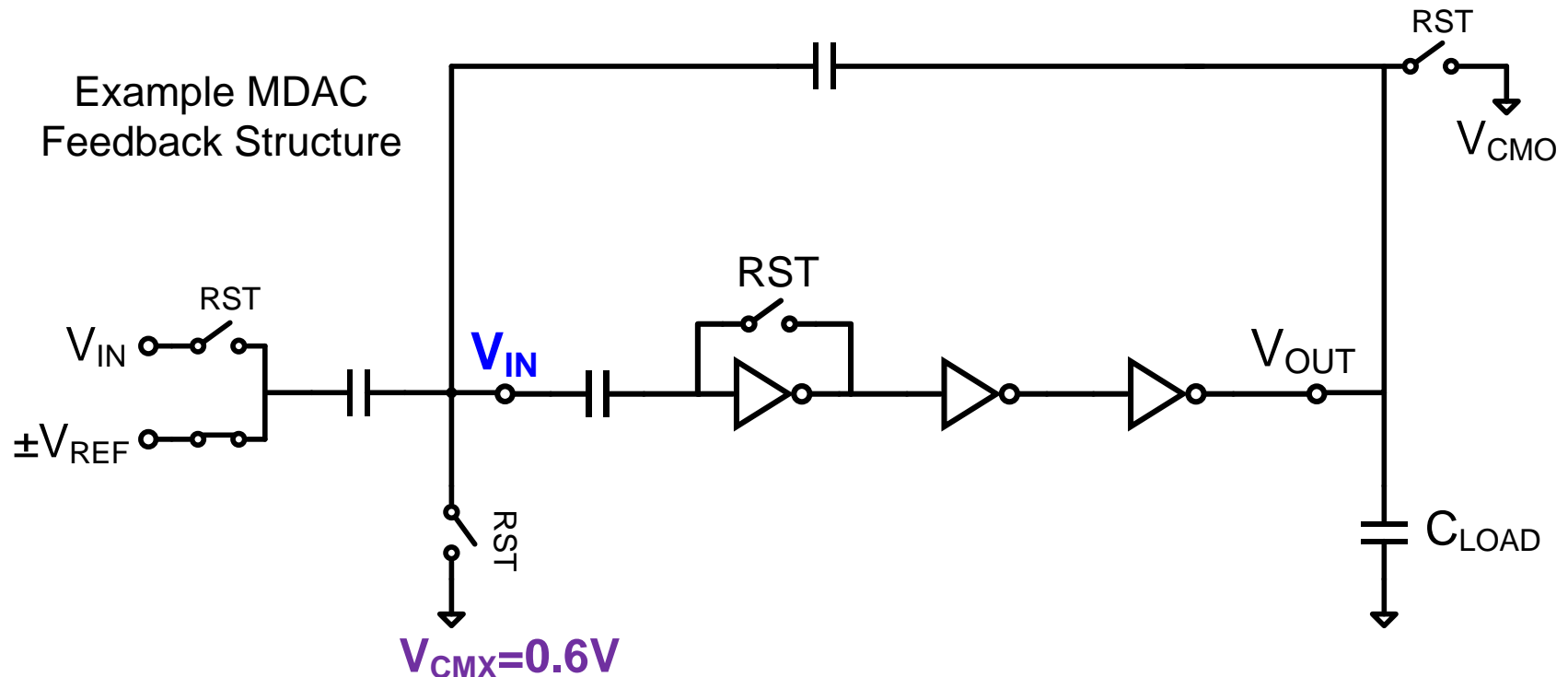


- Ring Oscillator
- Unstable...
...but will oscillate around the correct settled value

Ring Oscillator Sample Waveform

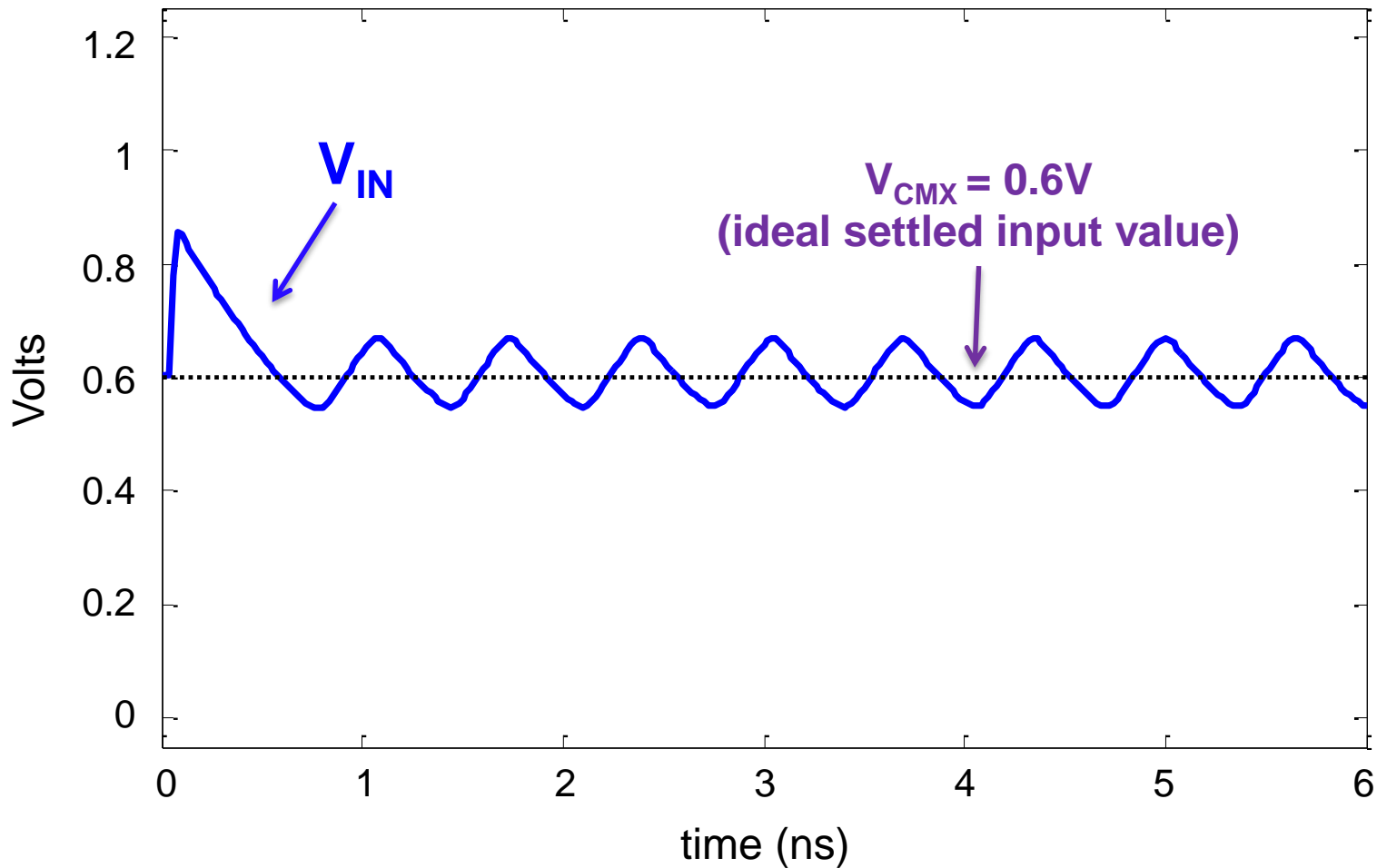


Ring Amplifier: Basic Theory

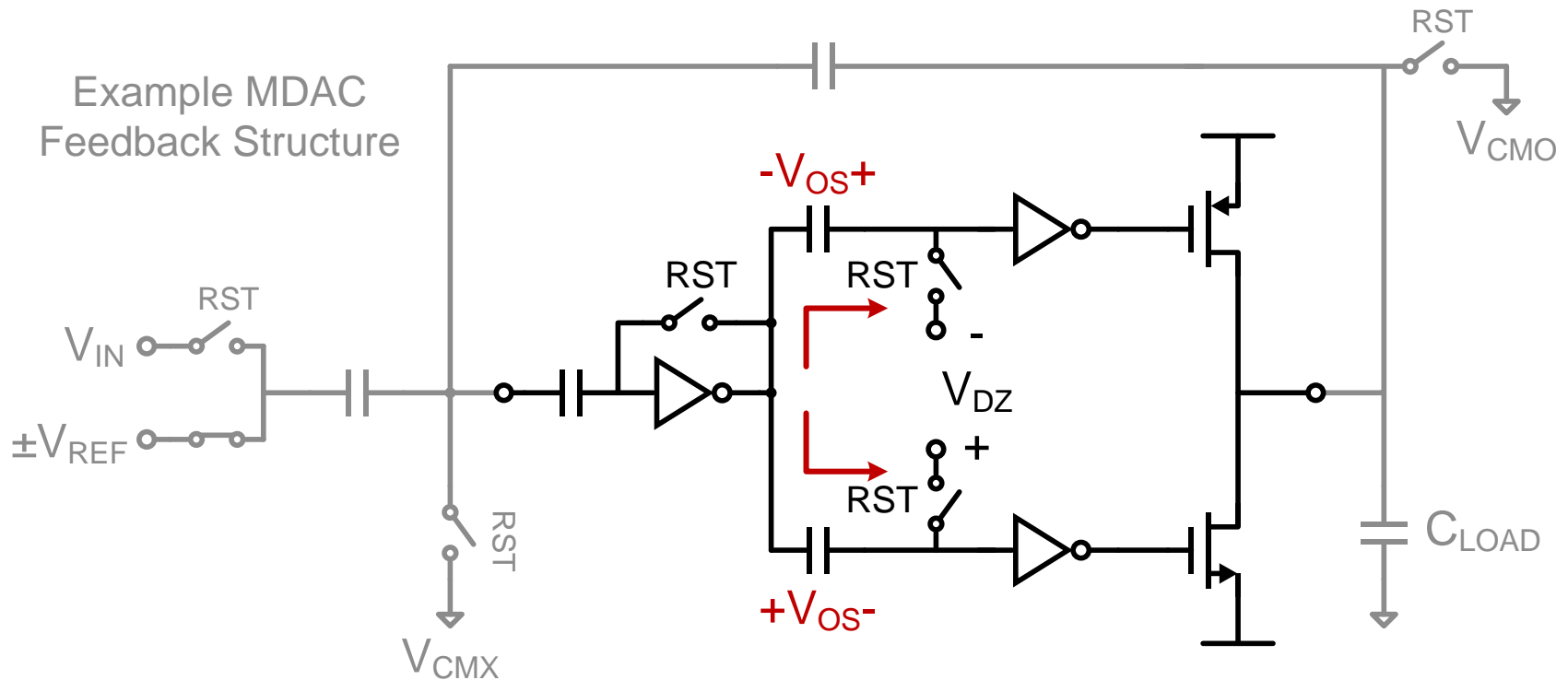

- Split signal into two separate paths
- Embed offset in each path


Ring Amplifier Sample Waveform

$V_{DZ} = 0\text{mV}$

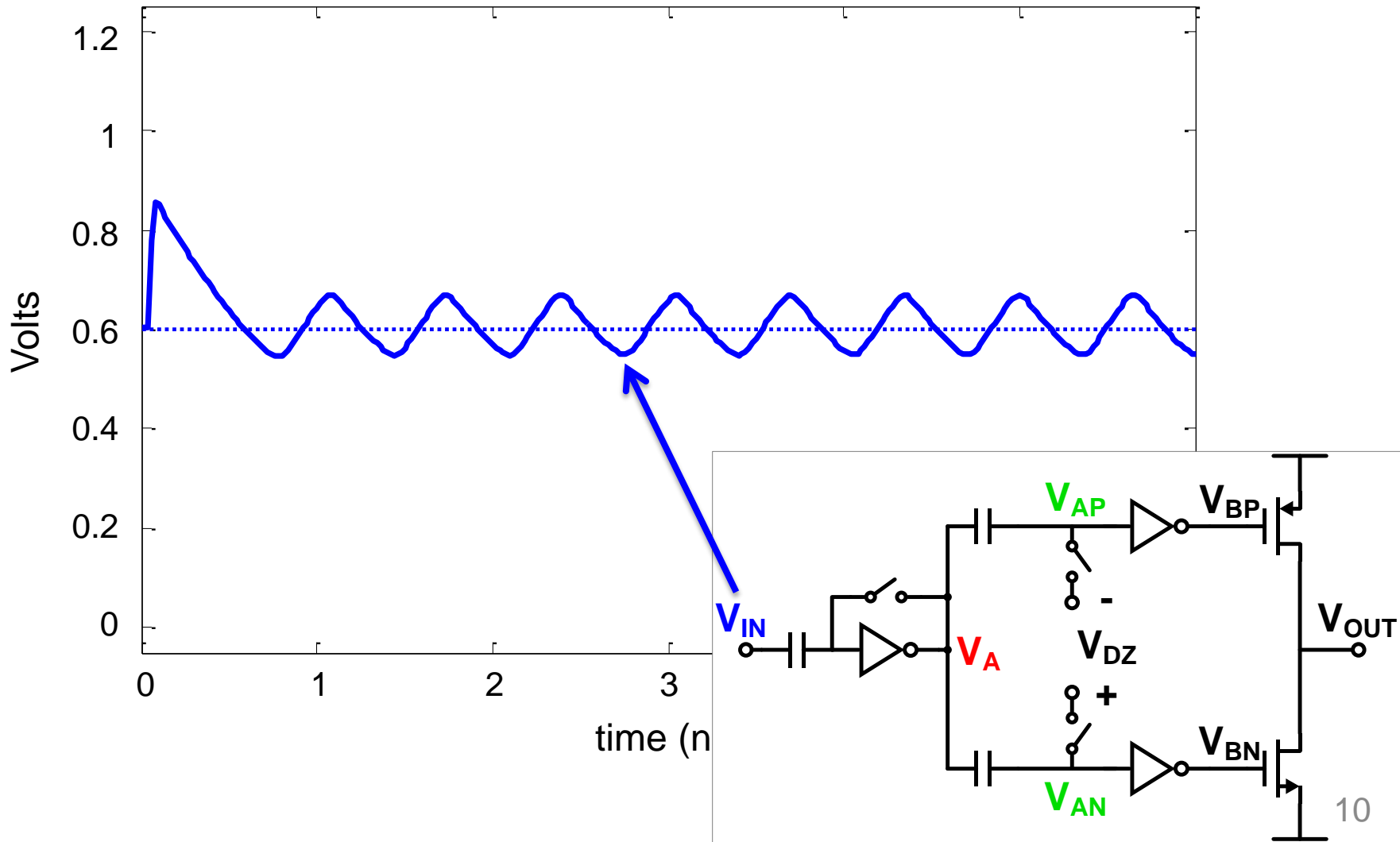


Ring Amplifier Sample Waveform

$V_{DZ} = 0\text{mV}$

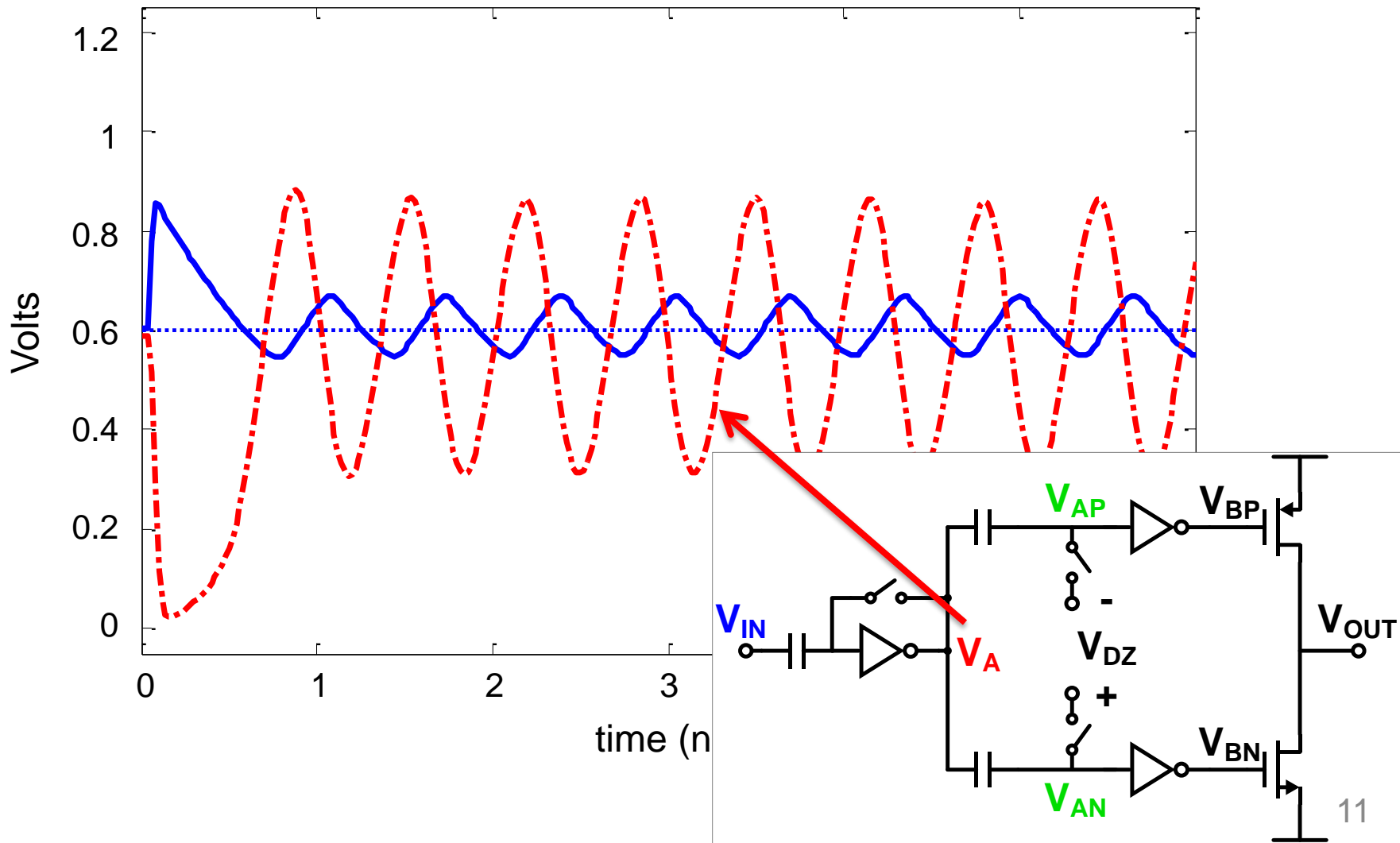


Ring Amplifier Sample Waveform

$V_{DZ} = 0\text{mV}$

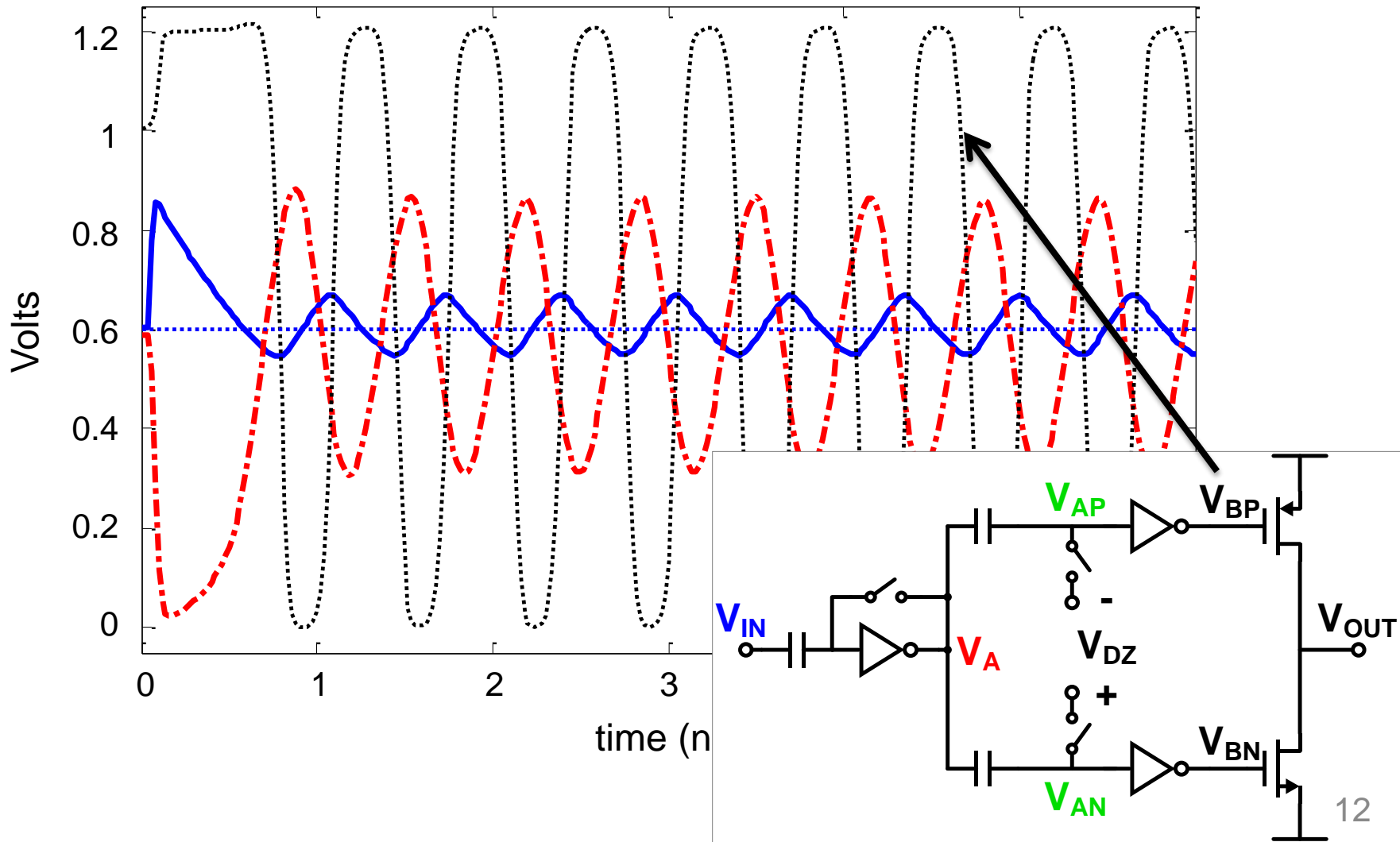


Ring Amplifier Sample Waveform

$V_{DZ} = 0\text{mV}$

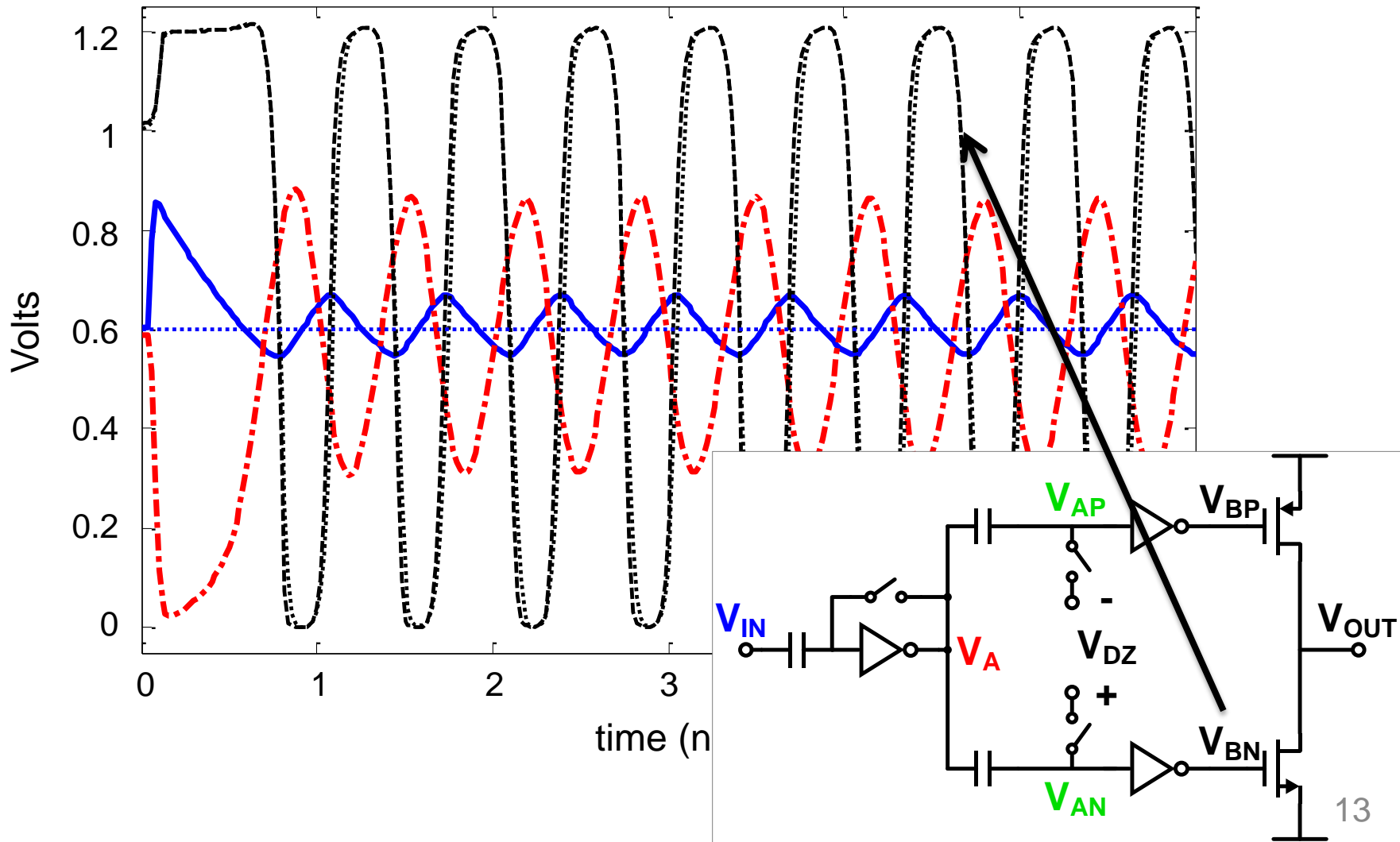

Ring Amplifier Sample Waveform


$V_{DZ} = 200\text{mV}$

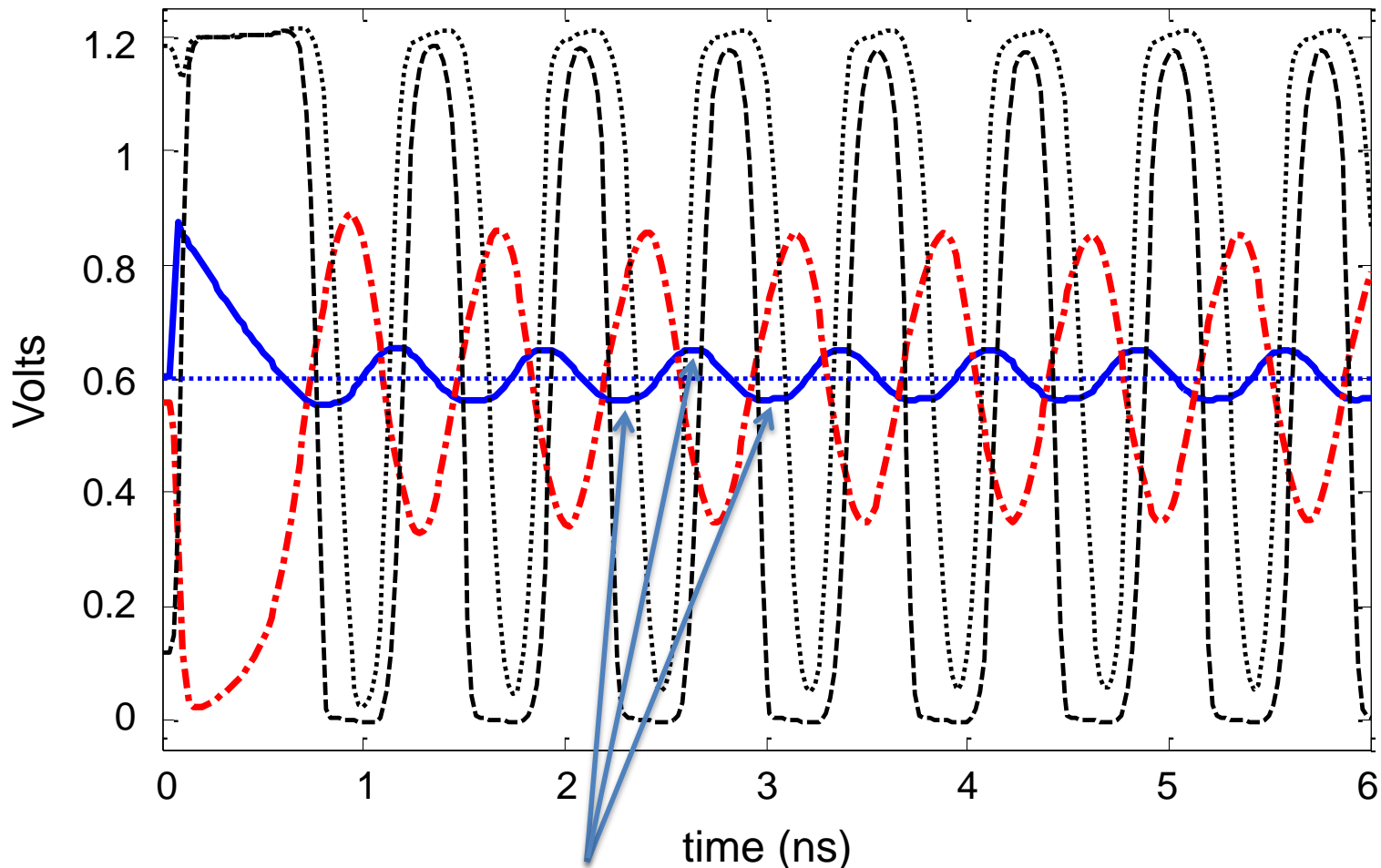

Plateaus form at dead-zone crossings


Ring Amplifier Sample Waveform

$V_{DZ} = 250\text{mV}$

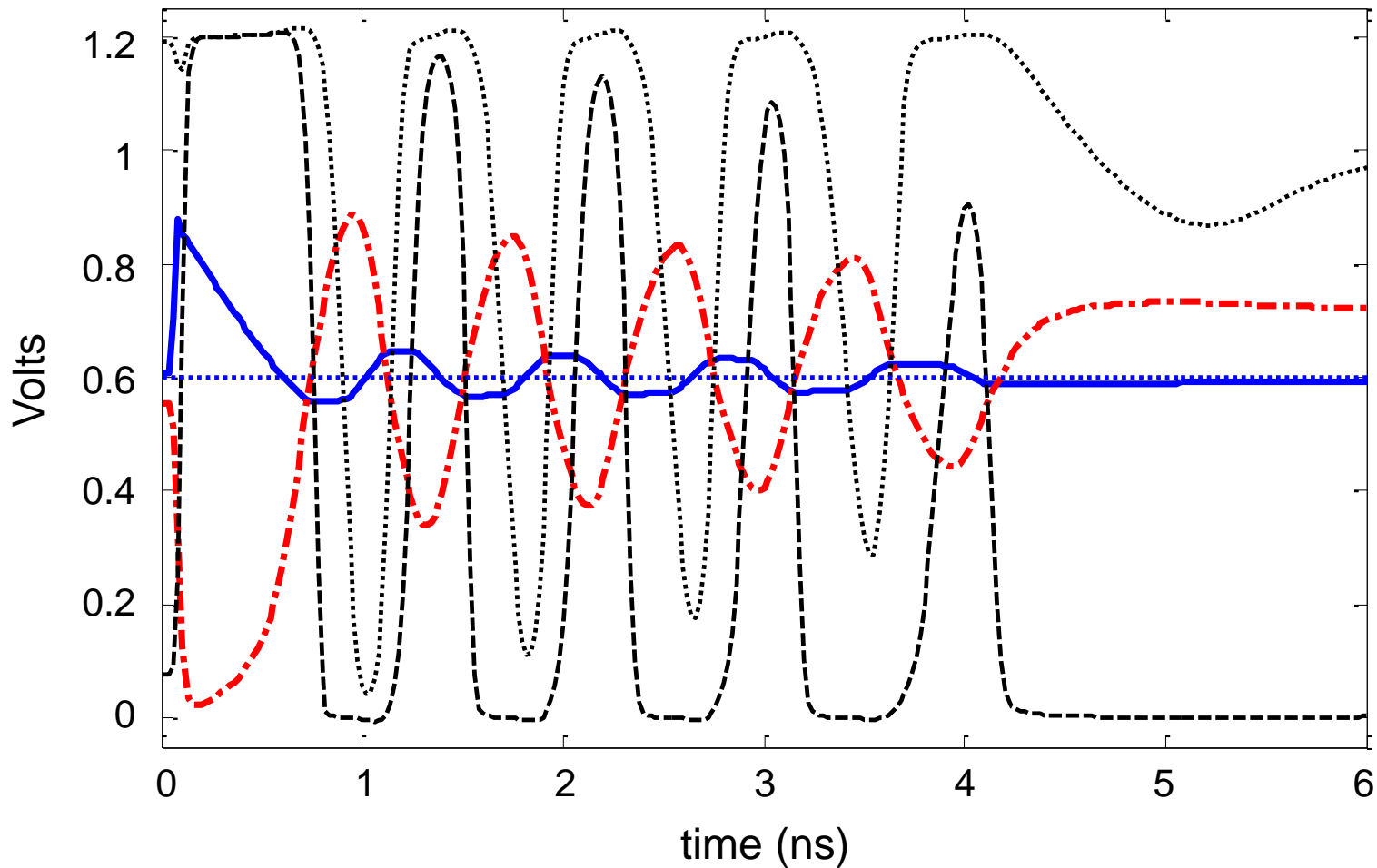


Ring Amplifier Sample Waveform

$V_{DZ} = 300\text{mV}$

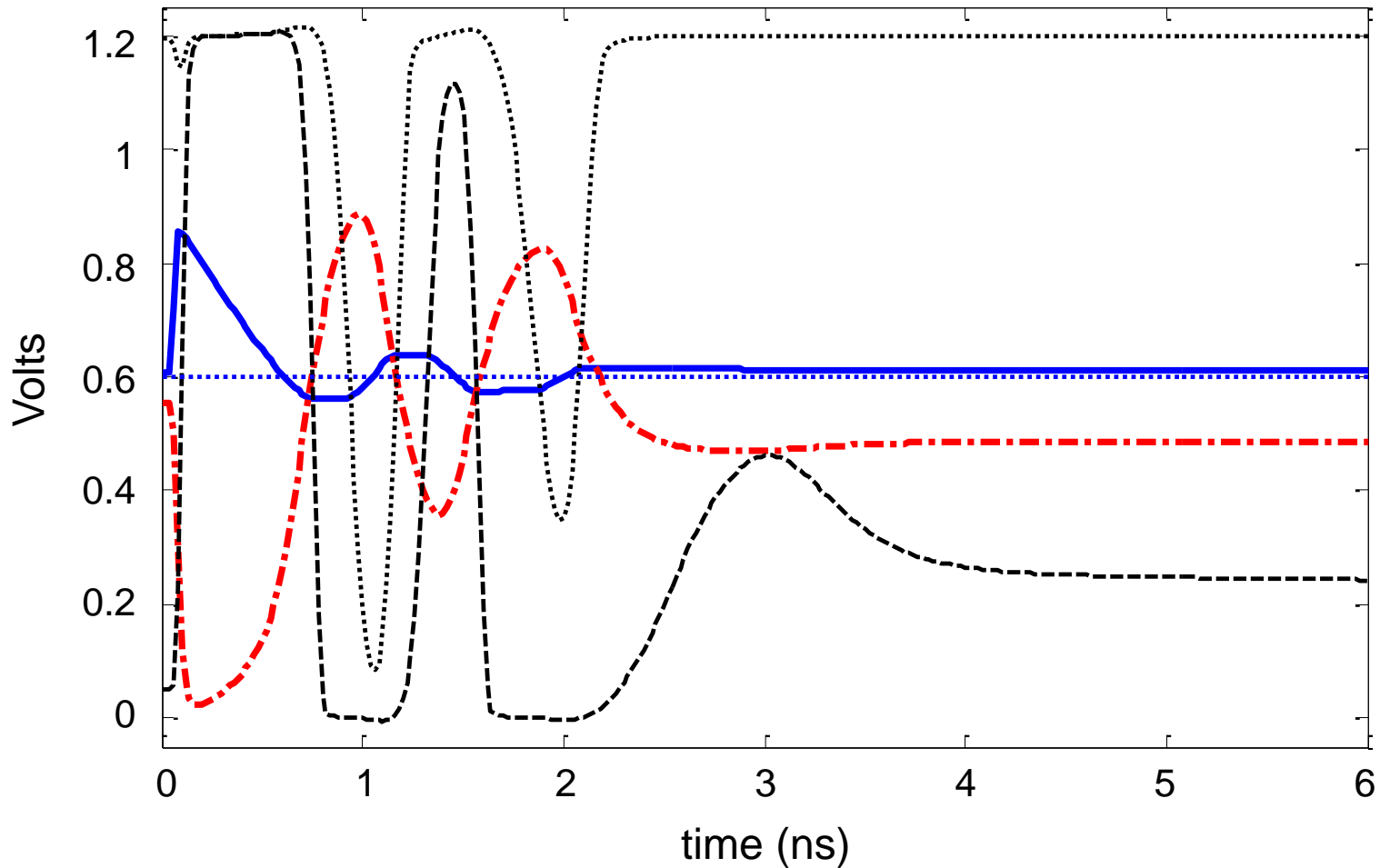


Ring Amplifier Sample Waveform

$V_{DZ} = 350\text{mV}$

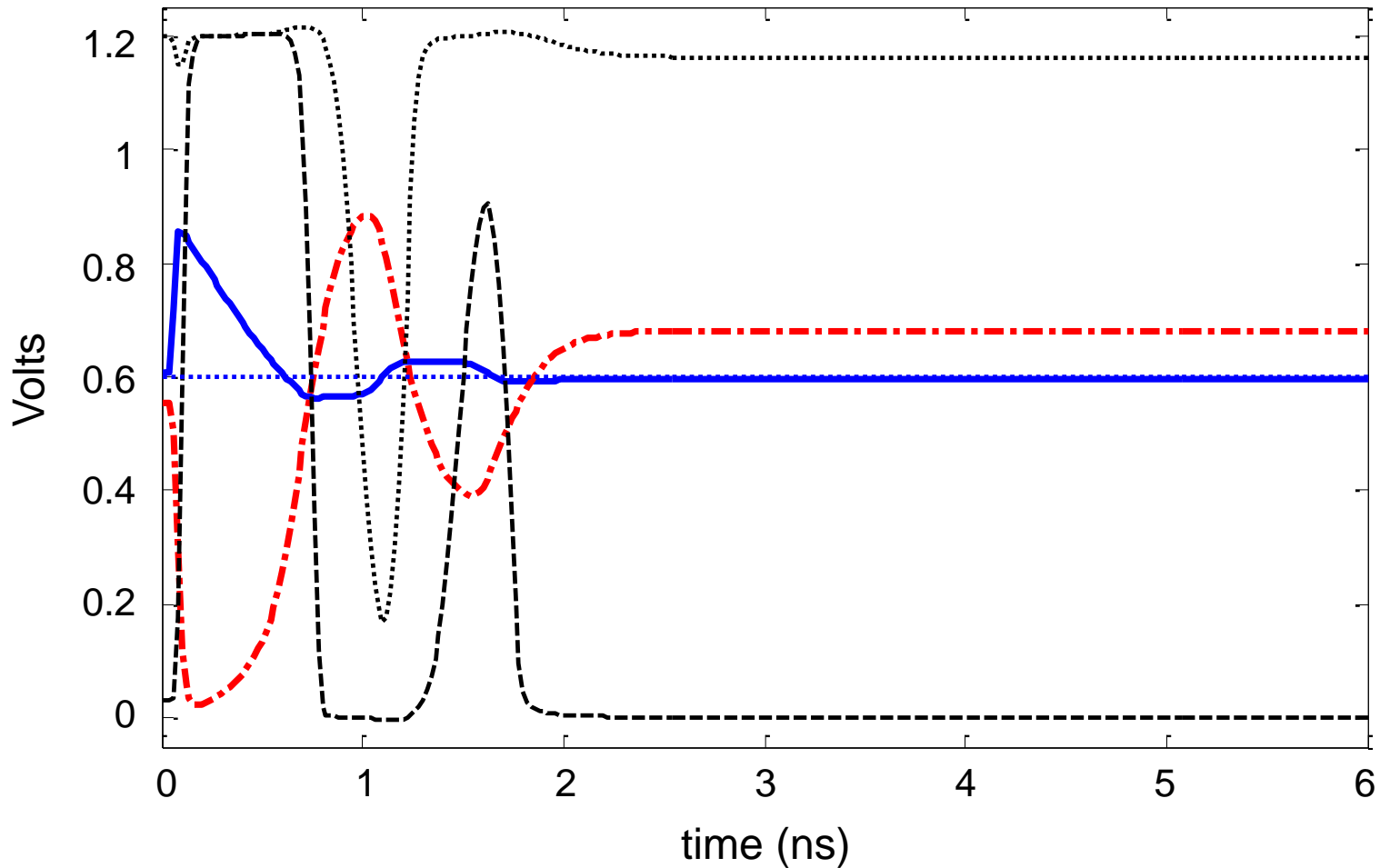


Ring Amplifier Sample Waveform

$V_{DZ} = 400\text{mV}$

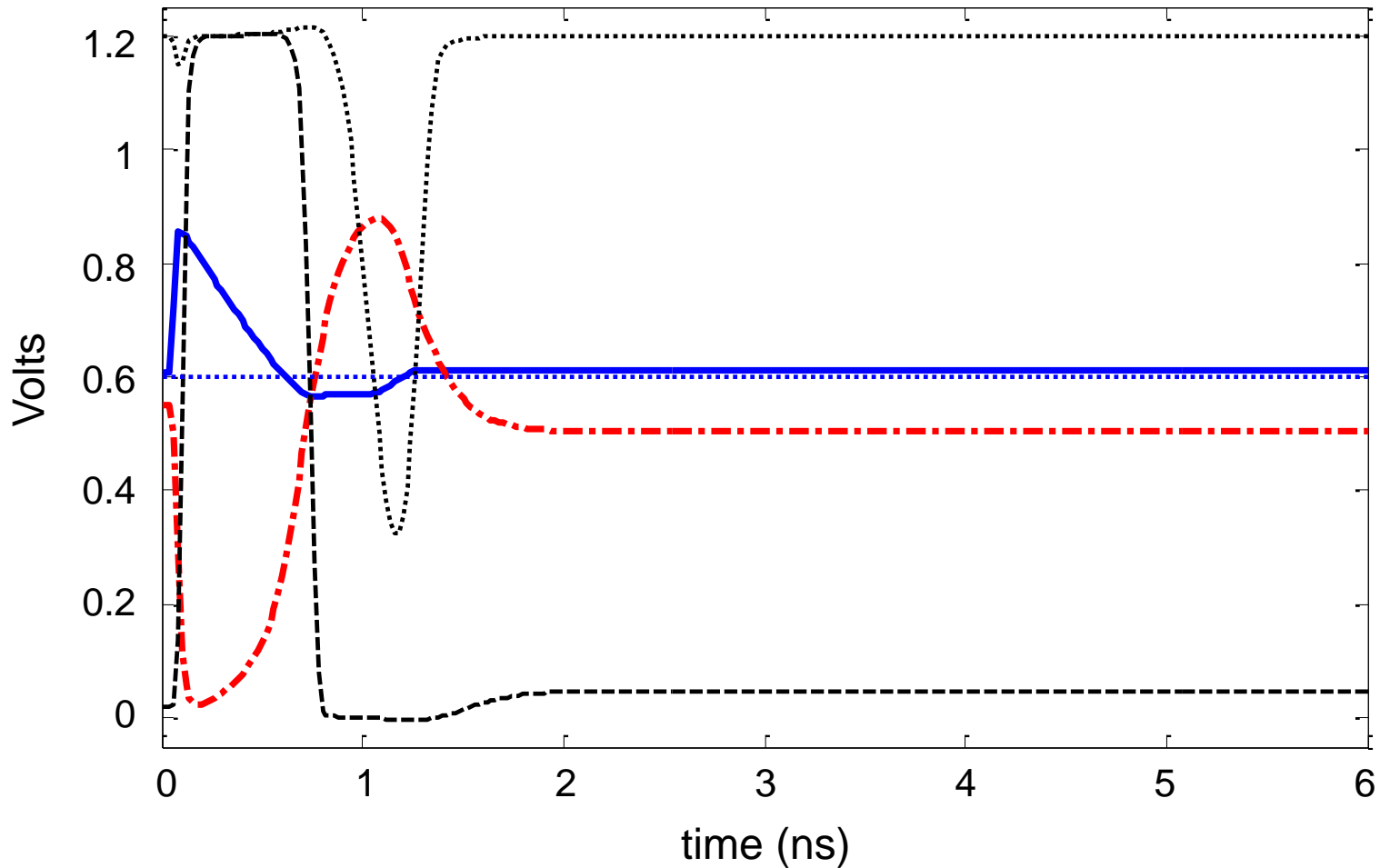


Ring Amplifier Sample Waveform

$V_{DZ} = 250\text{mV}$

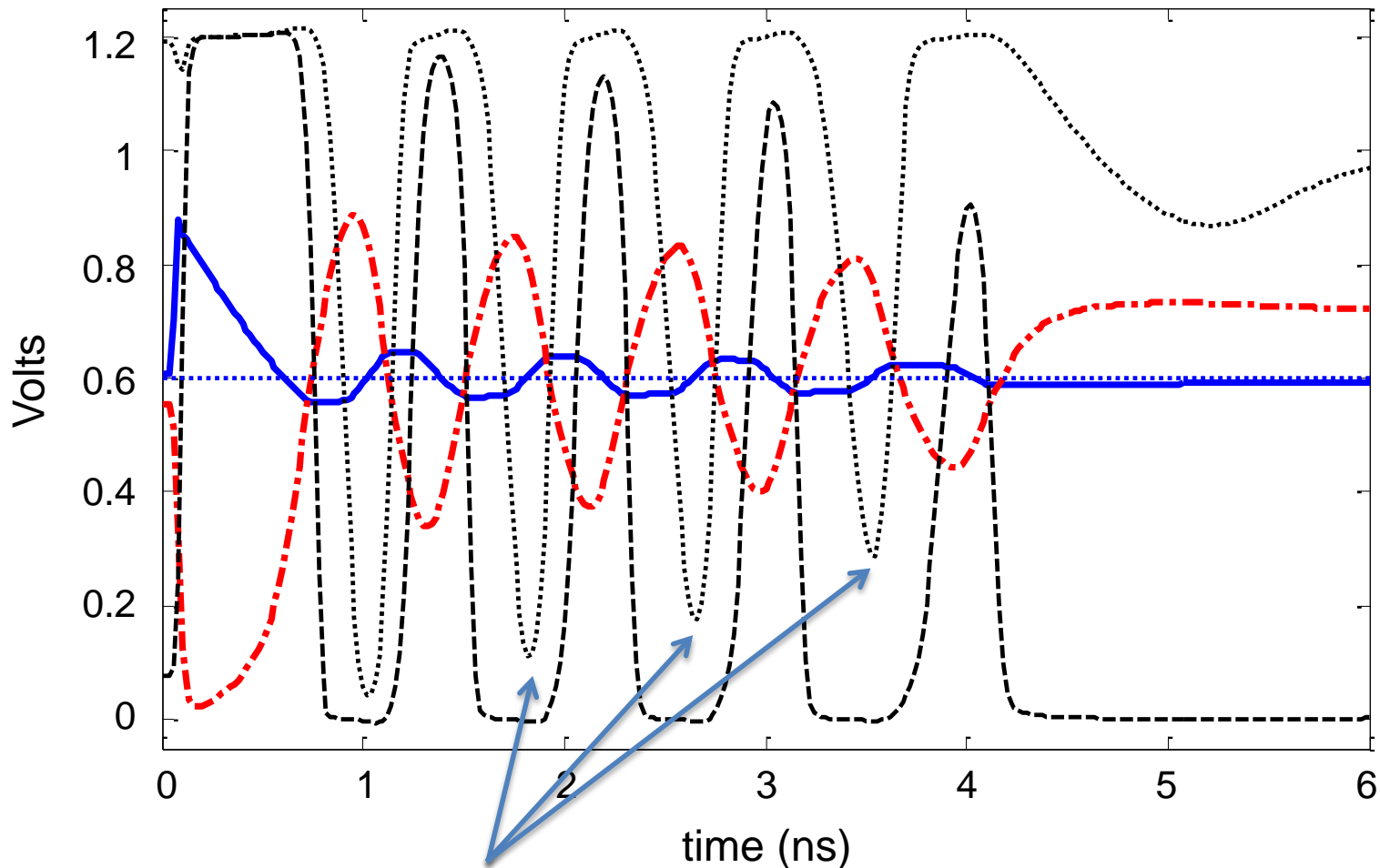


Decreasing V_{OV} reduces slew-rate

V_{OV} Dynamic Pinch-off

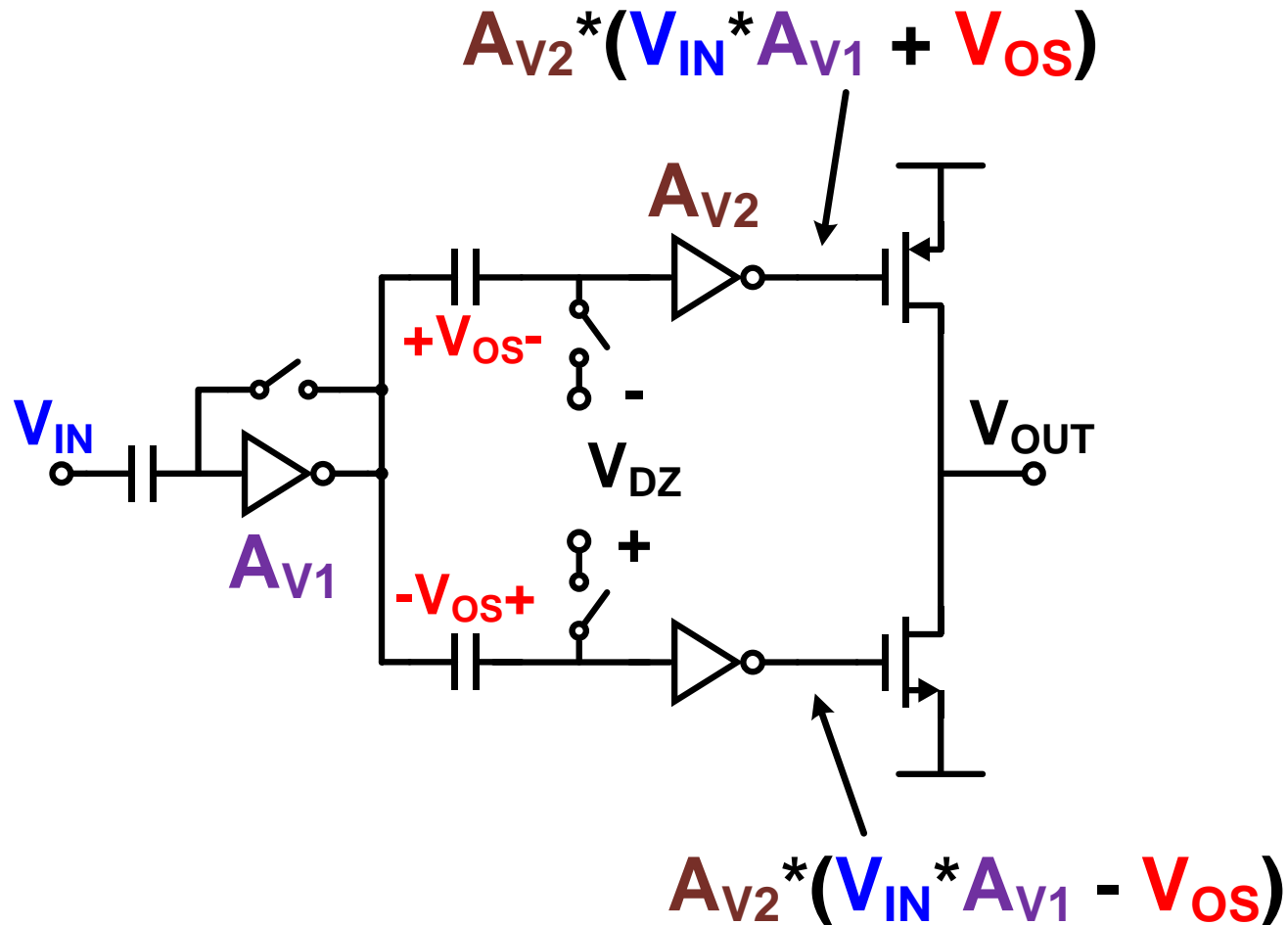


V_{OV} Dynamic Pinch-off

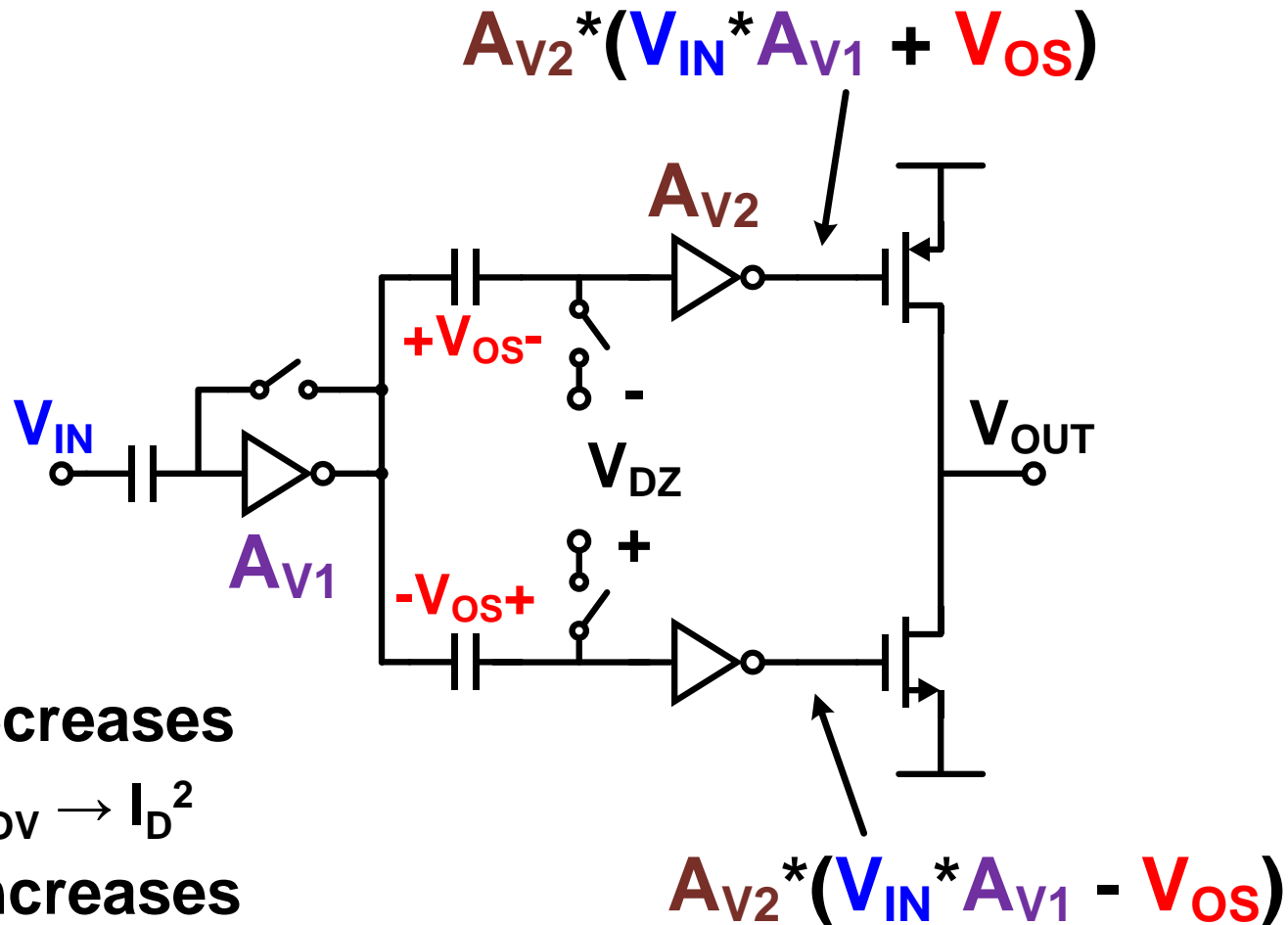

- I_D decreases
 - $V_{OV} \rightarrow I_D^2$
- R_o increases
 - Dominant pole \rightarrow DC

Dynamic Dead-zone Adjustment

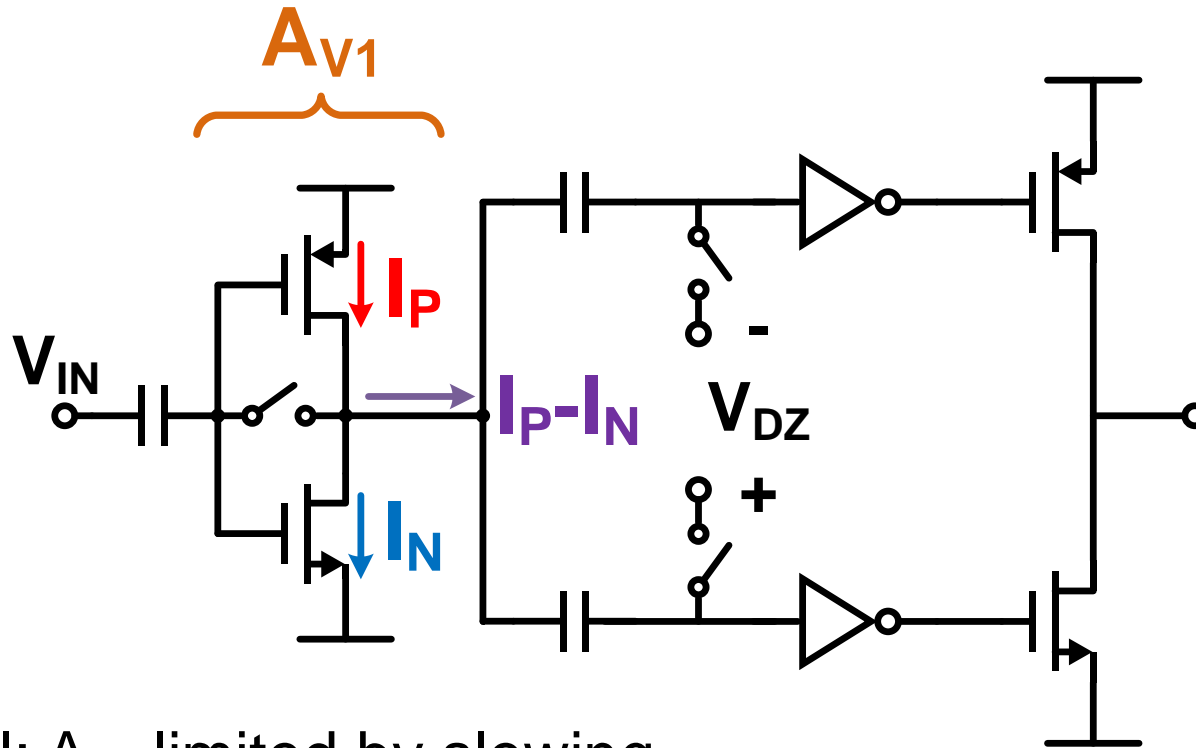

- Initial: A_{V1} limited by slewing
- Final: A_{V1} set by AC small-signal
- Dynamically adjusts input-referred dead-zone
- Enhances Speed / Accuracy trade-off

Core Benefits

Ring Amplifier Core Benefits


Slew-based charging

- Charges with maximally biased, digitally-switched current sources
 - Can be very small, even for large C_{LOAD}
 - Decouples internal speed vs. output load requirements

Ring Amplifier Core Benefits

Scalability (Speed/Power)

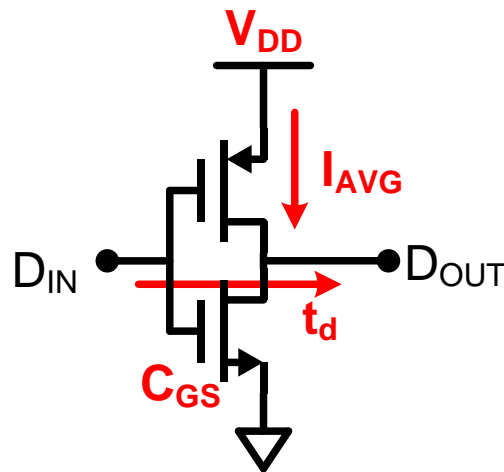- Internal speed/power (mostly) independent of C_{LOAD}
 - Inverter t_d , crowbar current, parasitic C's
 - Digital power-delay product scaling benefits apply
- Captures the same power/speed trends as digital circuits





$$PDP = V_{DD} \cdot I_{AVG} \cdot t_d = E_{tot}$$


Ring Amplifier Core Benefits

Scalability (Output Swing / SNR)

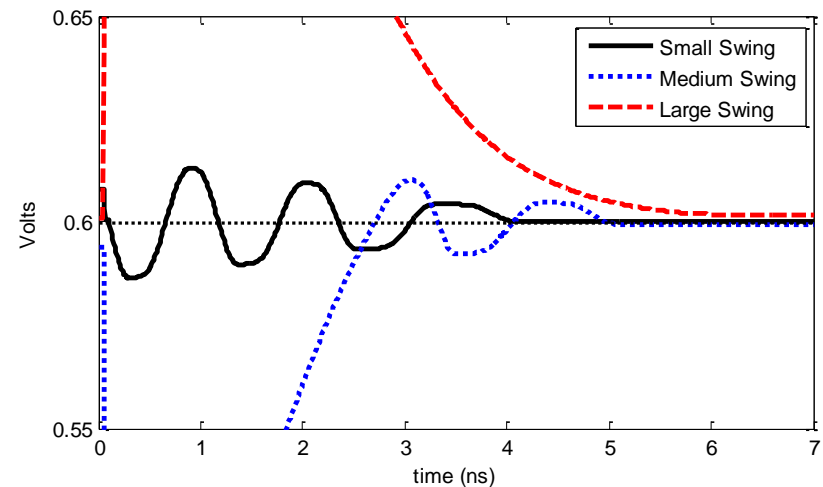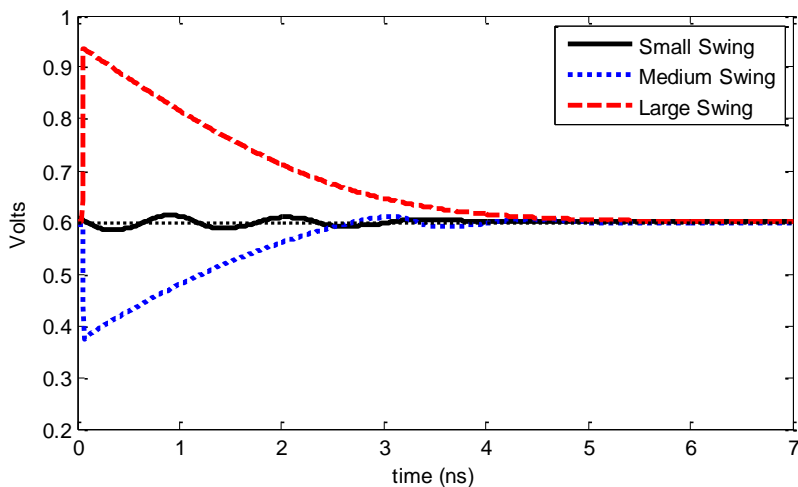- **Compression immune: rail-to-rail output swing**
- 50dB: Input-referred dead-zone size will limit accuracy
- 90dB: dynamic pinch-off effects maintain high accuracy
 - weak inversion
 - saturation even for small V_{DS}
 - gain-boosting from increased r_o




Noise Suppression

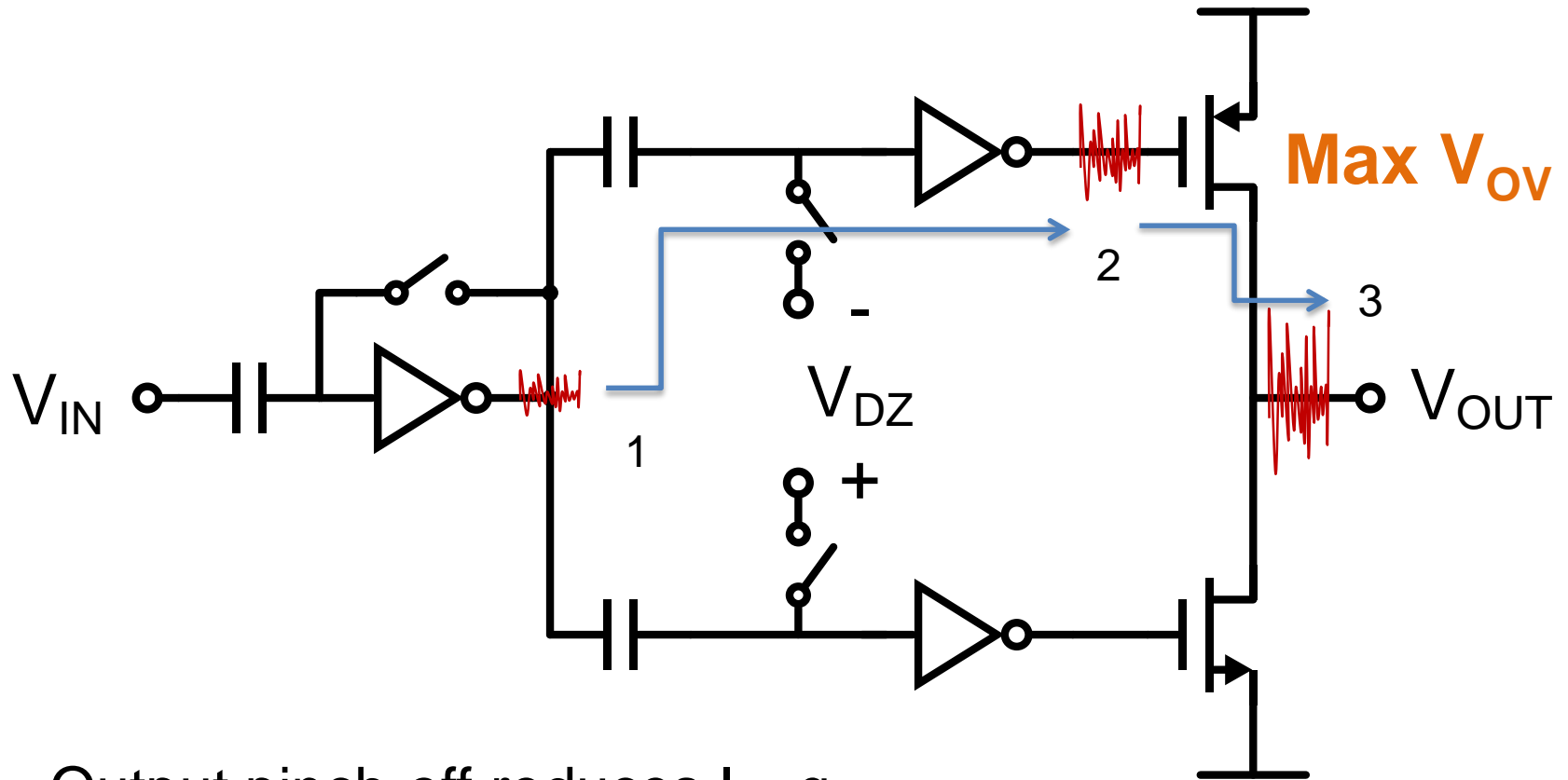

- Output pinch-off reduces I_D , g_m
 - Internal noise sources attenuated
- Initial charging noisy \rightarrow final settling quiet


Noise Suppression

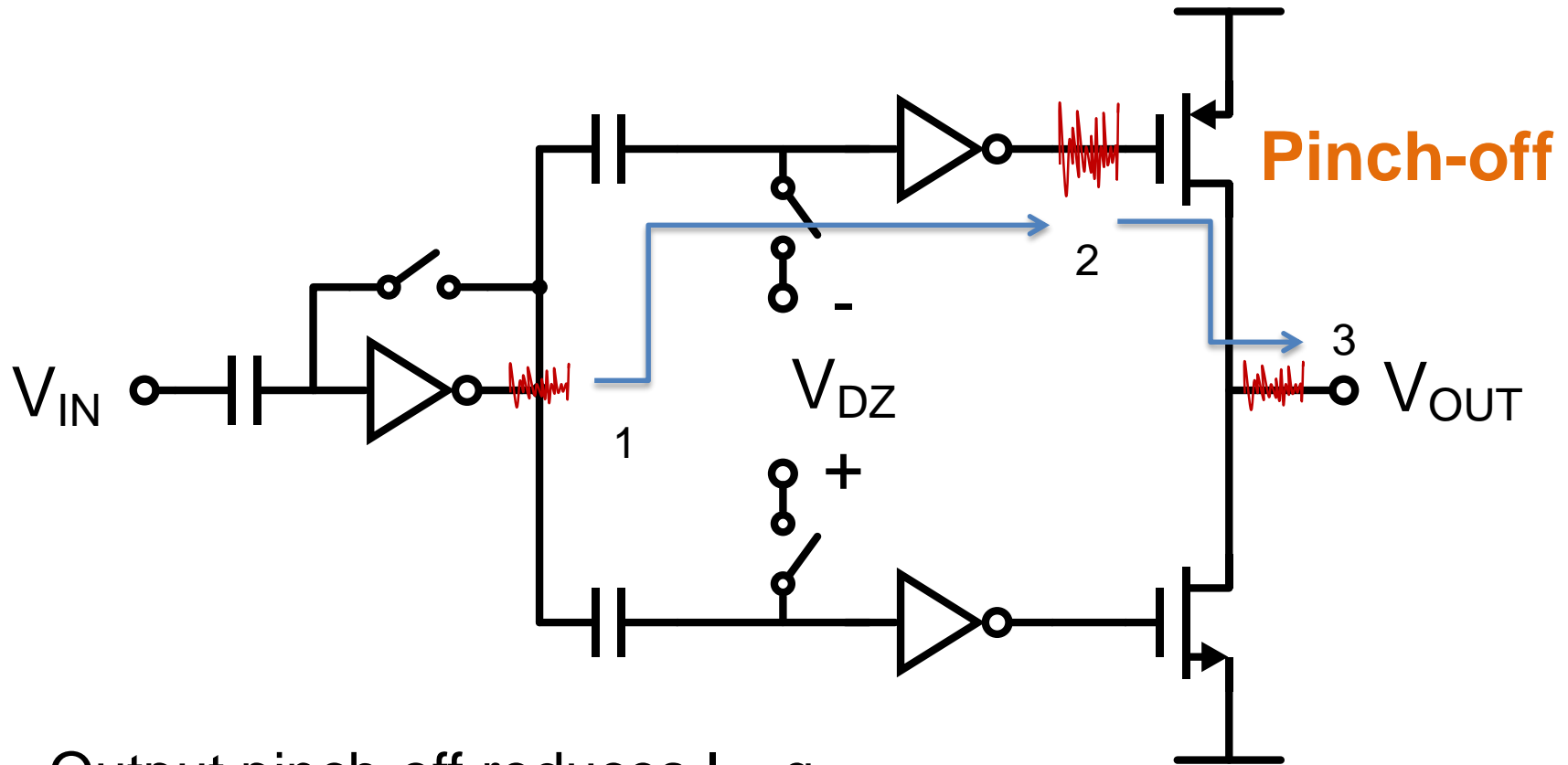

- Output pinch-off reduces I_D , g_m
 - Internal noise sources attenuated
- Initial charging noisy \rightarrow final settling quiet


ADC Implementation Details

Structure Overview

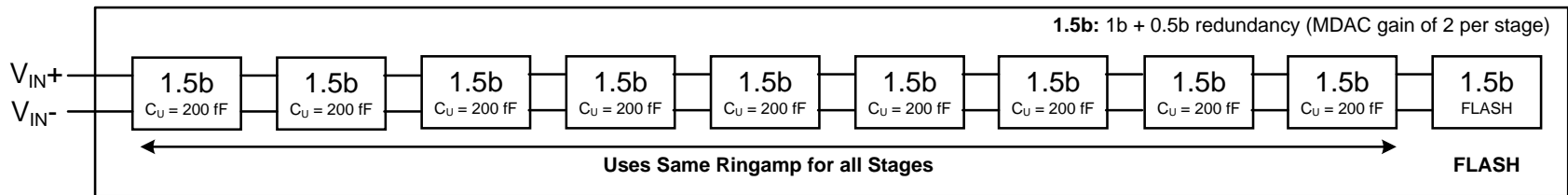


- 10.5b Pipelined ADC
 - 9 identical 1.5b MDAC stages
 - 1.5b Flash
- Simple proof-of-concept built to characterize:
 - Basic functionality
 - Rail-to-rail output swing
 - Noise immunity

Ring amplifier

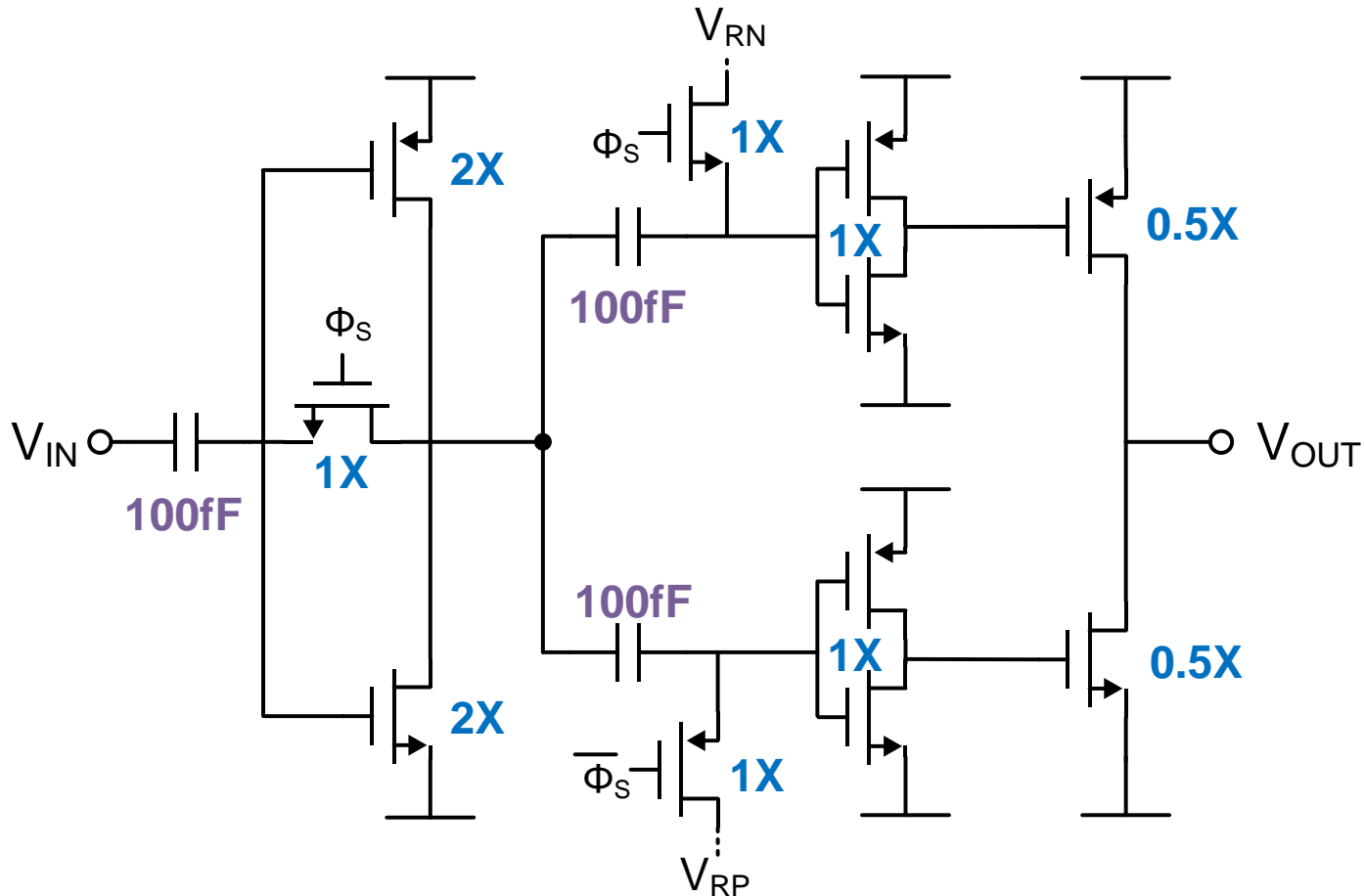


- Very small, very simple, uses minimum size inverters

Float-sampled MDAC

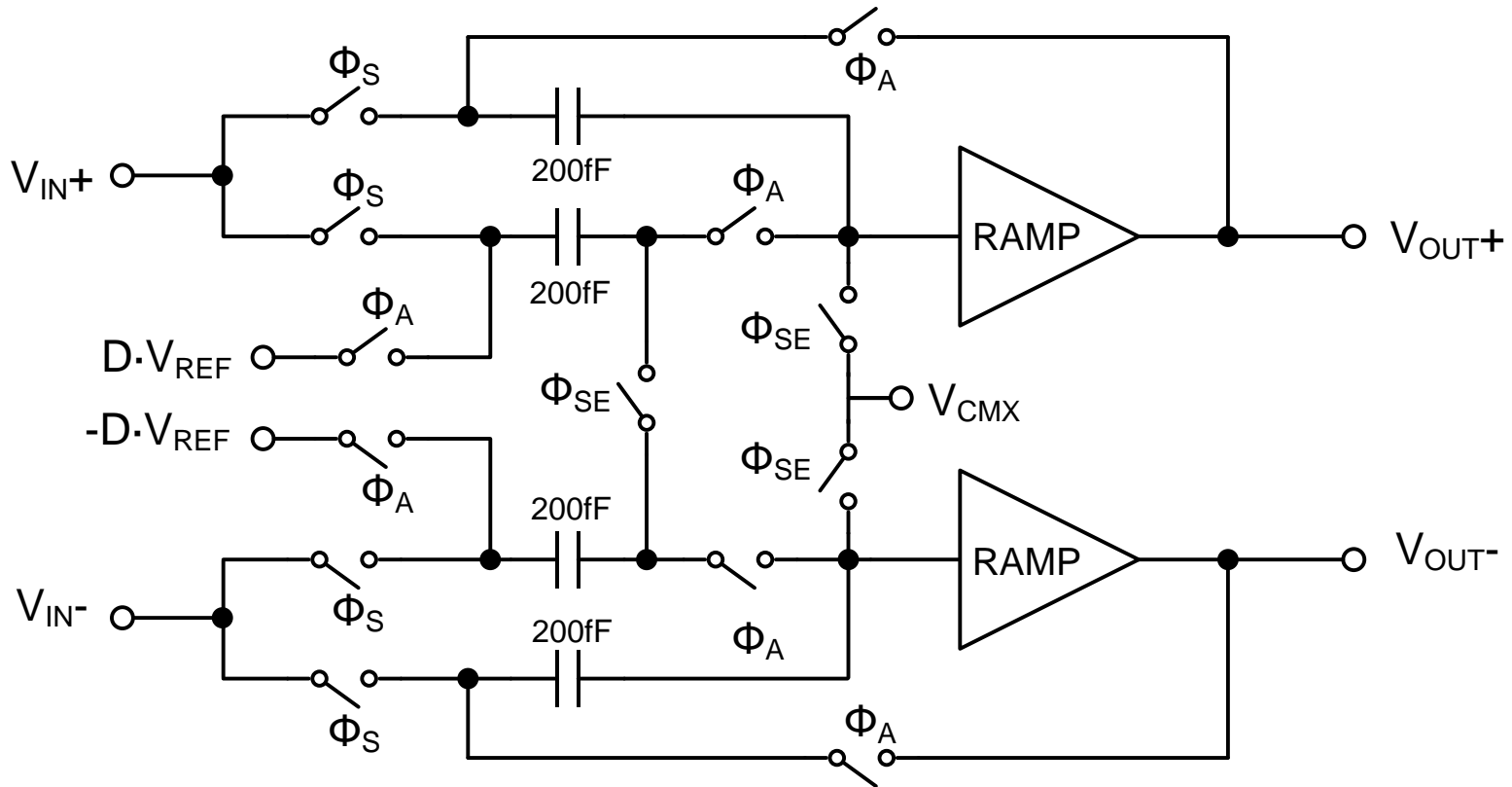


- Differential gain: 2X
- Common-mode gain: 1X

Measurement Results

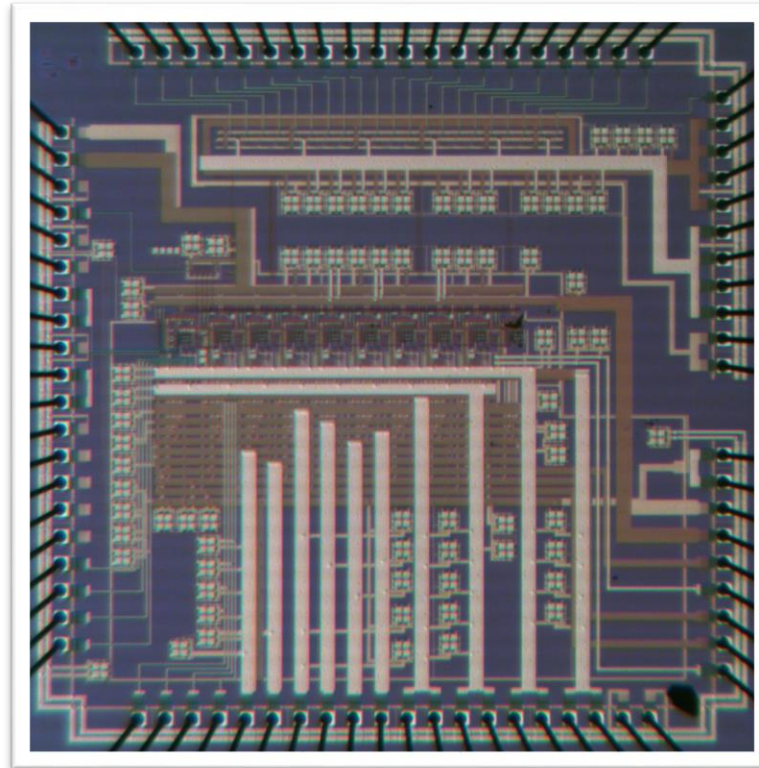


Input Spectrum

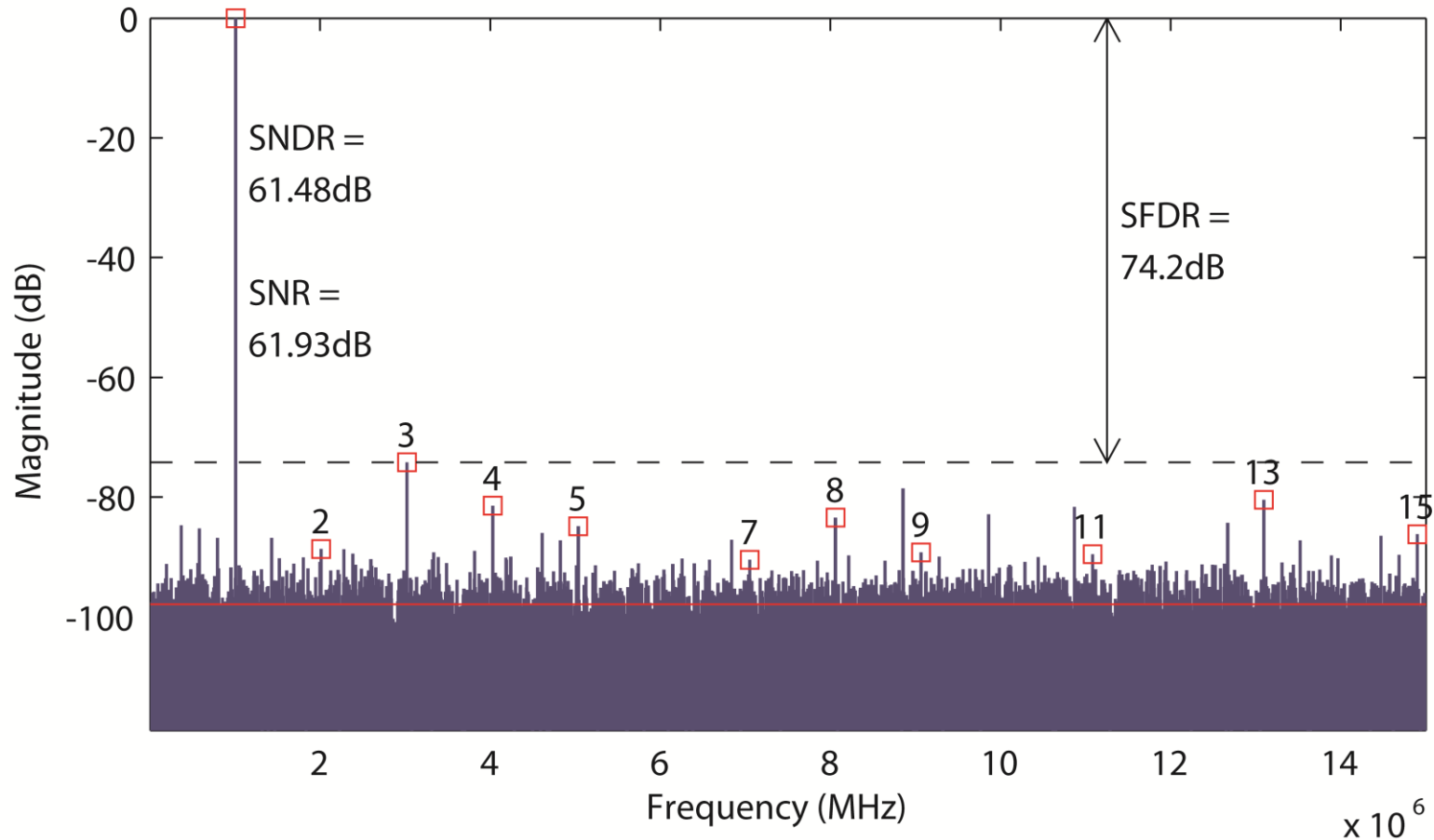


- Limited by quantization noise
- Inherent noise advantage demonstrated

Rail-to-Rail Output Swing Test

Rail-to-rail output swing test

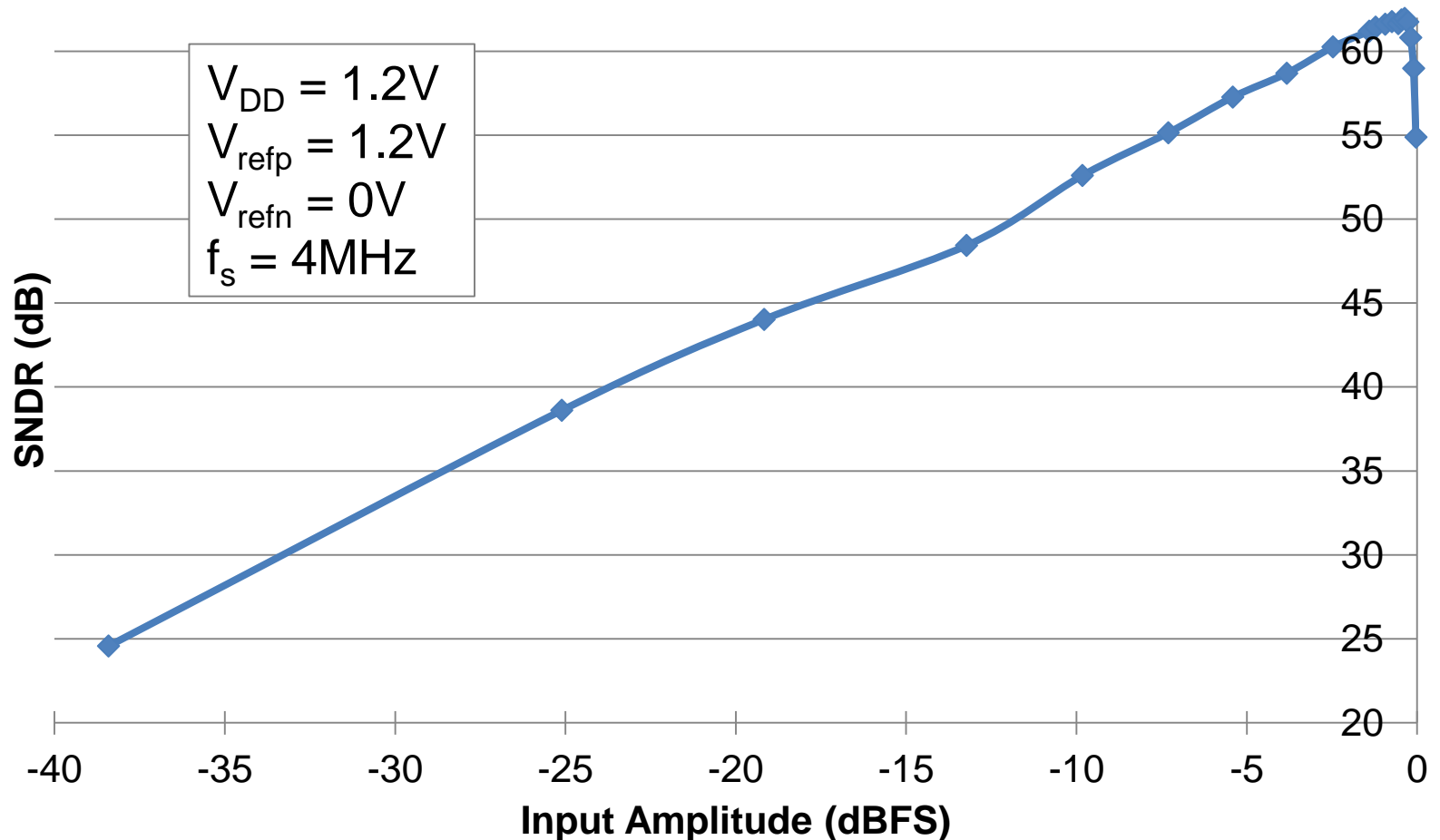

Ring Amp Dead-Zone Sensitivity

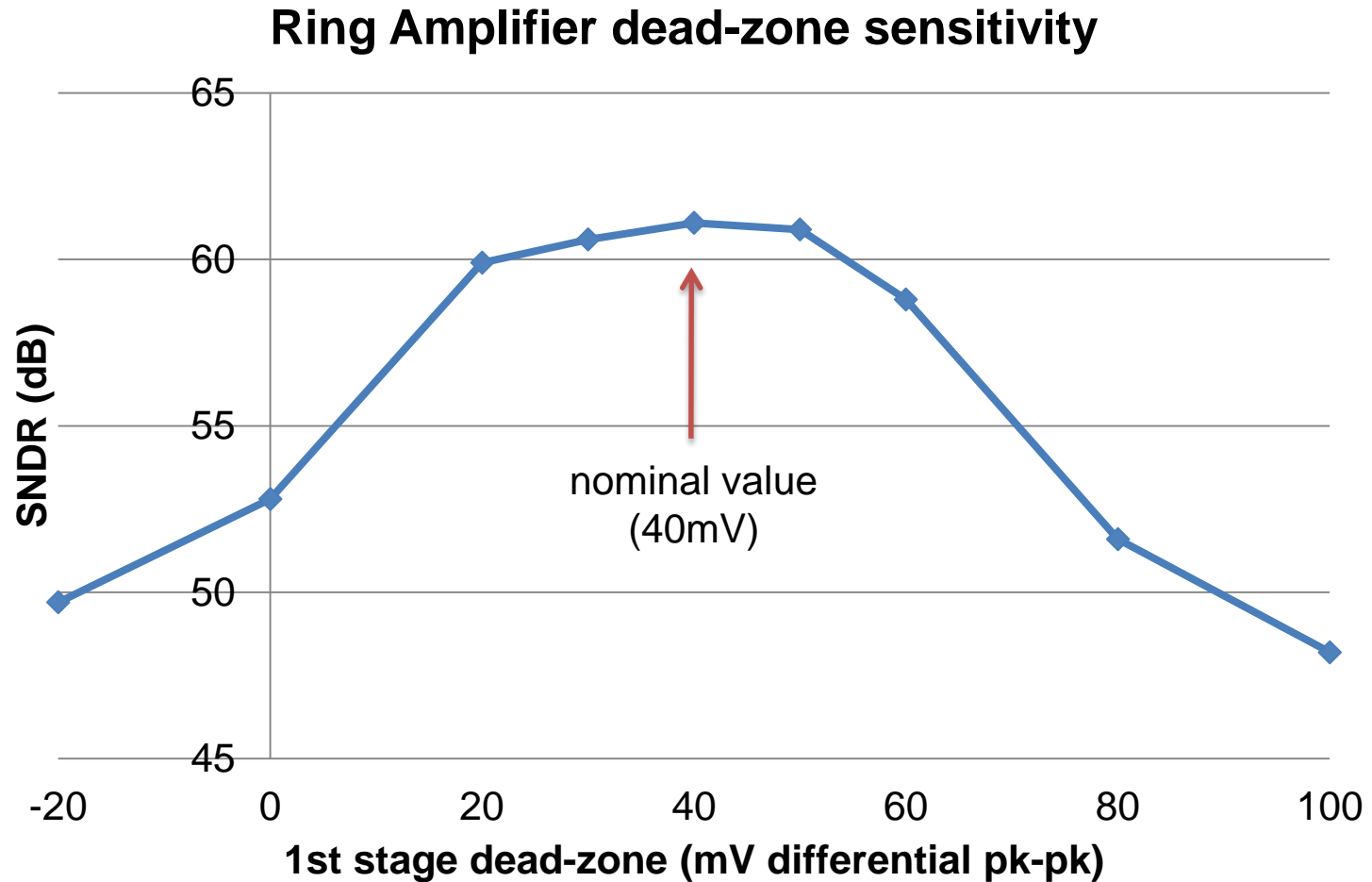

Performance Summary

Technology	0.18 μ m 1P4M CMOS
Resolution	10.5 bits
Analog Supply	1.3 V
Sampling rate	30 Msps
ERBW	15 MHz
Input Range	2.2 V pk-pk diff.
SNDR	61.5 dB
SNR	61.9 dB
SFDR	74.2 dB
ENOB	9.9 bits
Total Power	2.6 mW
FoM	90 fJ/c-step

Room for improvement

- Design meant to probe THD, SNR limits of minimum sized ringamp
 - Speed set intentionally low
 - No optimization, stage scaling
 - Ringamps left ‘on’ during sampling phase
 - FoM can easily be improved
- ISSCC 2012 implementation**
 - Speed: 90Msps
 - Power save features: 50% reduction in power


** B. Hershberg, et al. “Ring Amplifiers for Switched Capacitor Circuits”, ISSCC 2012

Scalability Test

- Design Challenge:
 - MDAC for 11b pipelined ADC with 10b ENOB
 - 130nm, 90nm, 65nm, 45nm, 32nm


V_{DD}	process defined
SNDR	> 66dB (input referred)
Output Swing	$0.8V_{DD}$
Total Load	800fF
Speed	proportional to $1/L_{min}$
Power	Minimize
- ASU predictive technology models [ptm.asu.edu]

Scalability Test

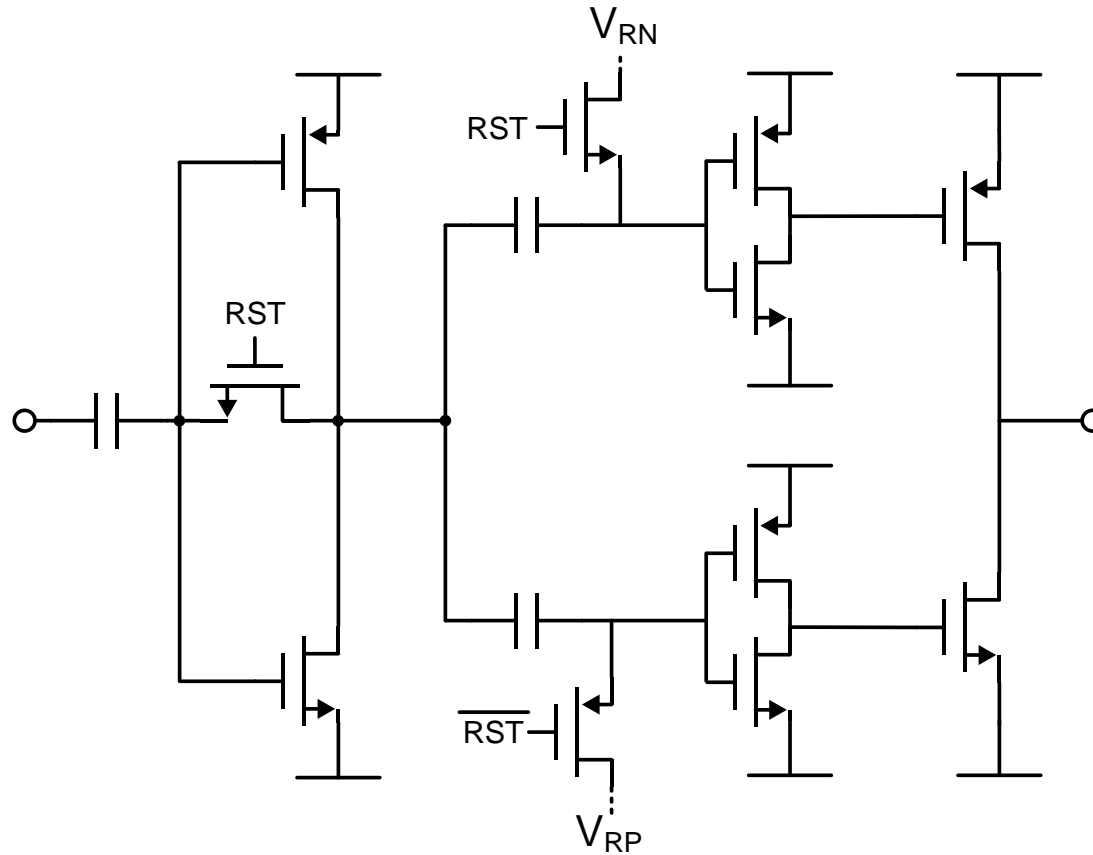


Test Ringamp

Scalability Test

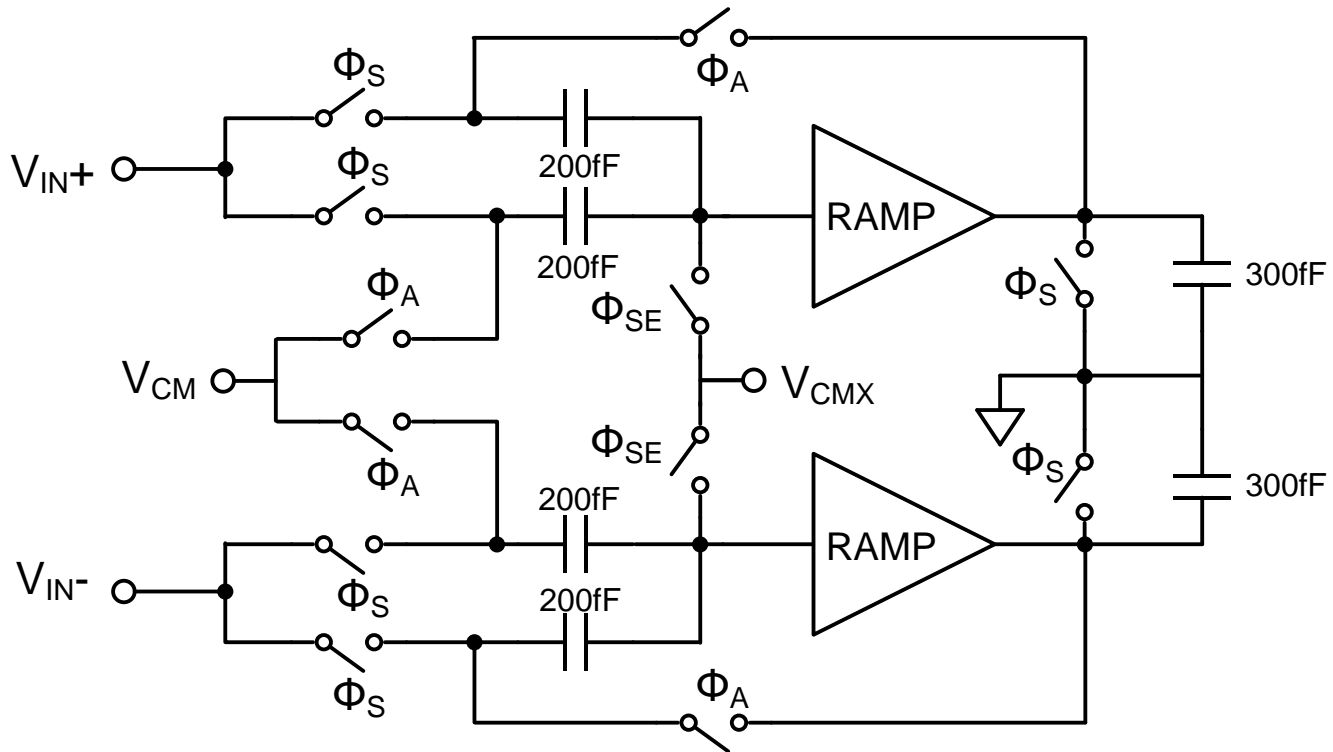

Pseudo-differential Test MDAC

Scalability Test

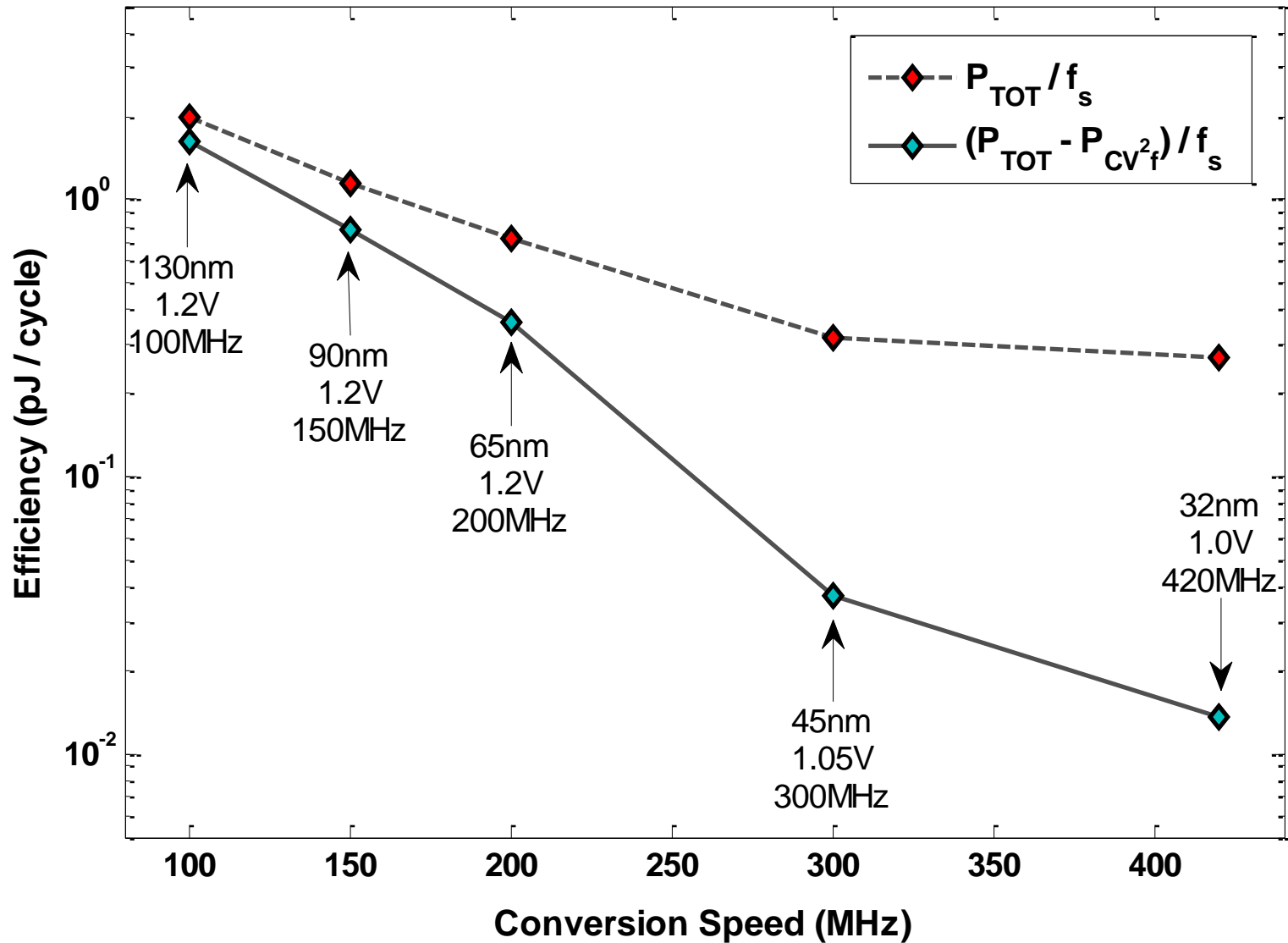

Conclusion


- Ring Amplification
 - High efficiency slew-based charging
 - Rail-to-rail output swing
 - Noise advantage
 - Performance scales with digital process
- Key Concepts
 - Dead-zone
 - V_{OV} pinch-off
 - Dynamic gain adjustment

Thank you for your attention

Additional Slides


Possibly useful in Q&A afterwards

Performance vs. Input Frequency

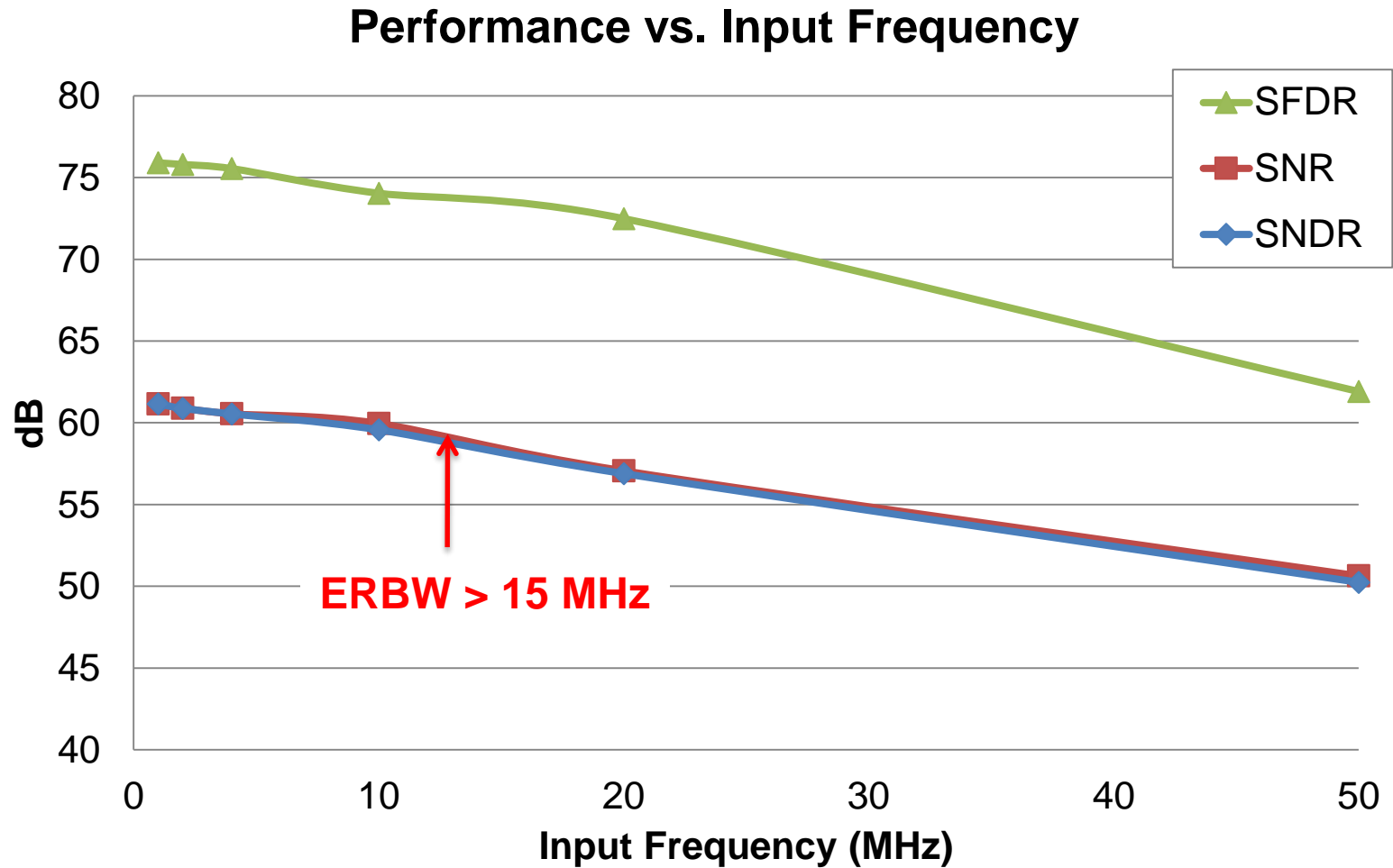


SNDR vs. Input Amplitude

SNDR vs Input Amplitude

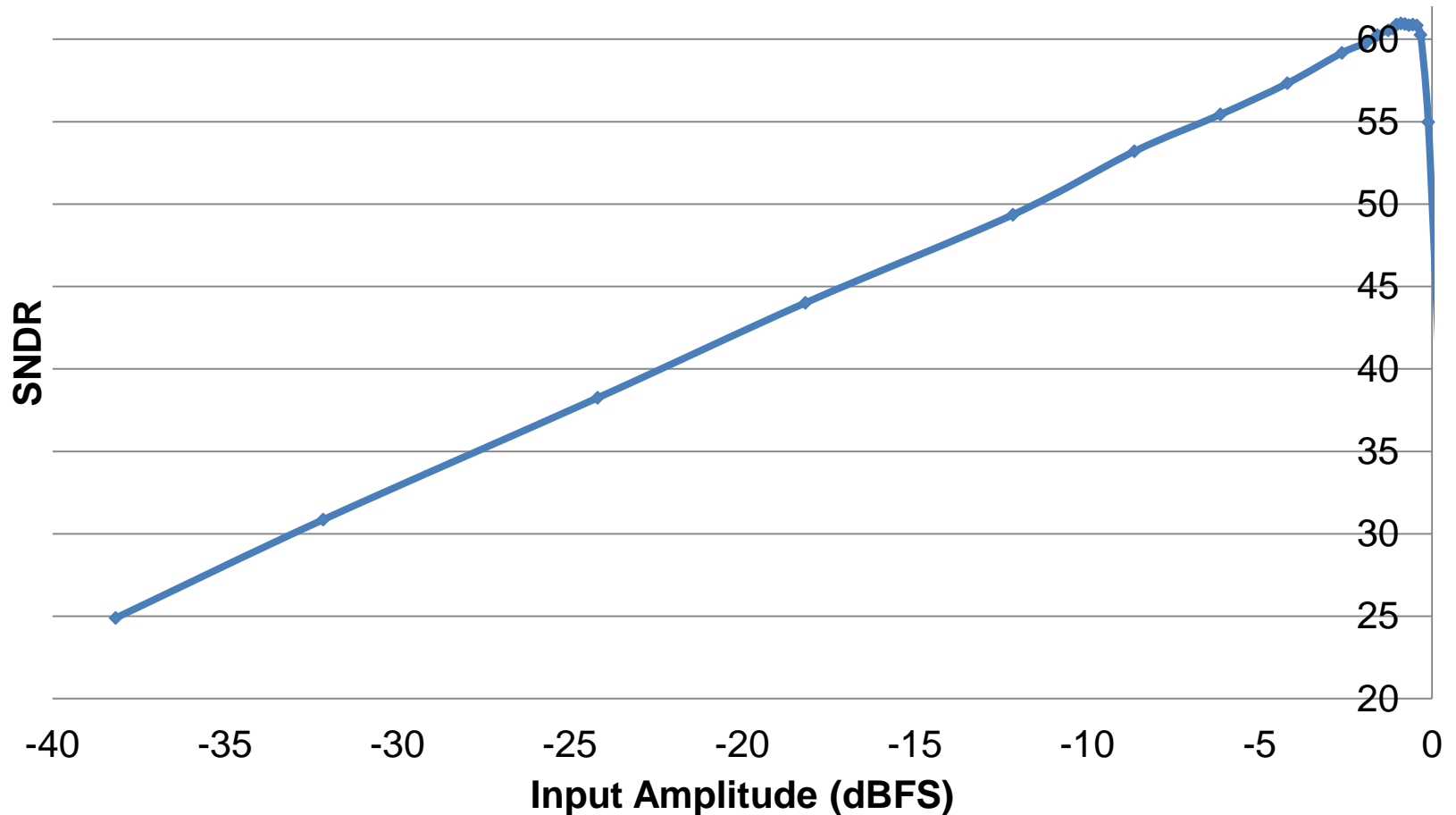


SNDR vs. Sampling Frequency

SNDR vs Sampling Frequency

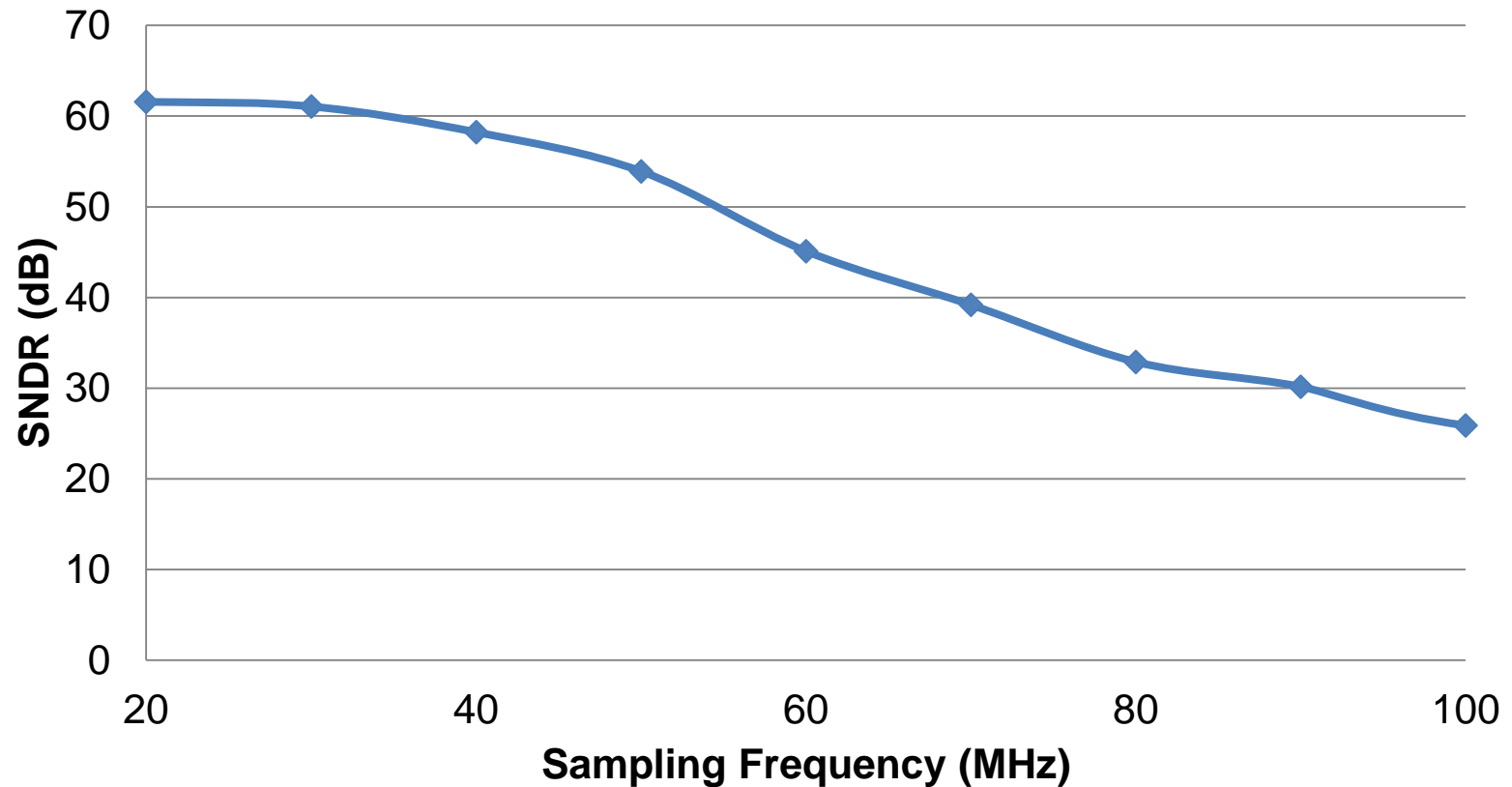


INL / DNL

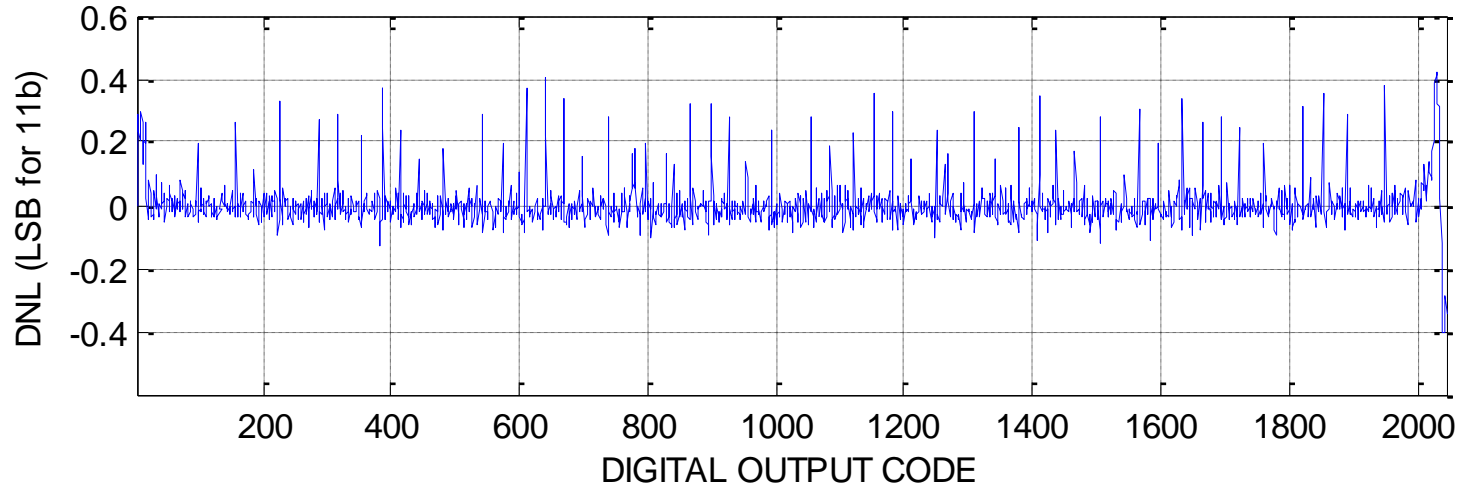DIFFERENTIAL NONLINEARITY vs. DIGITAL OUTPUT CODE




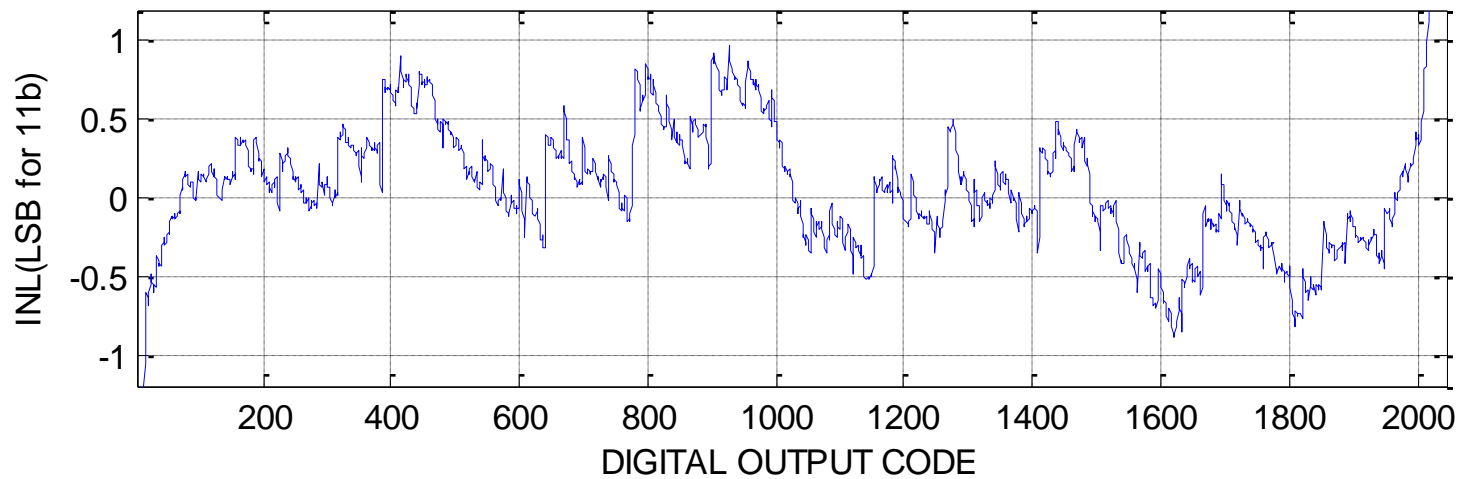INTEGRAL NONLINEARITY vs. DIGITAL OUTPUT CODE




SNDR vs. Sampling Frequency

SNDR vs Sampling Frequency

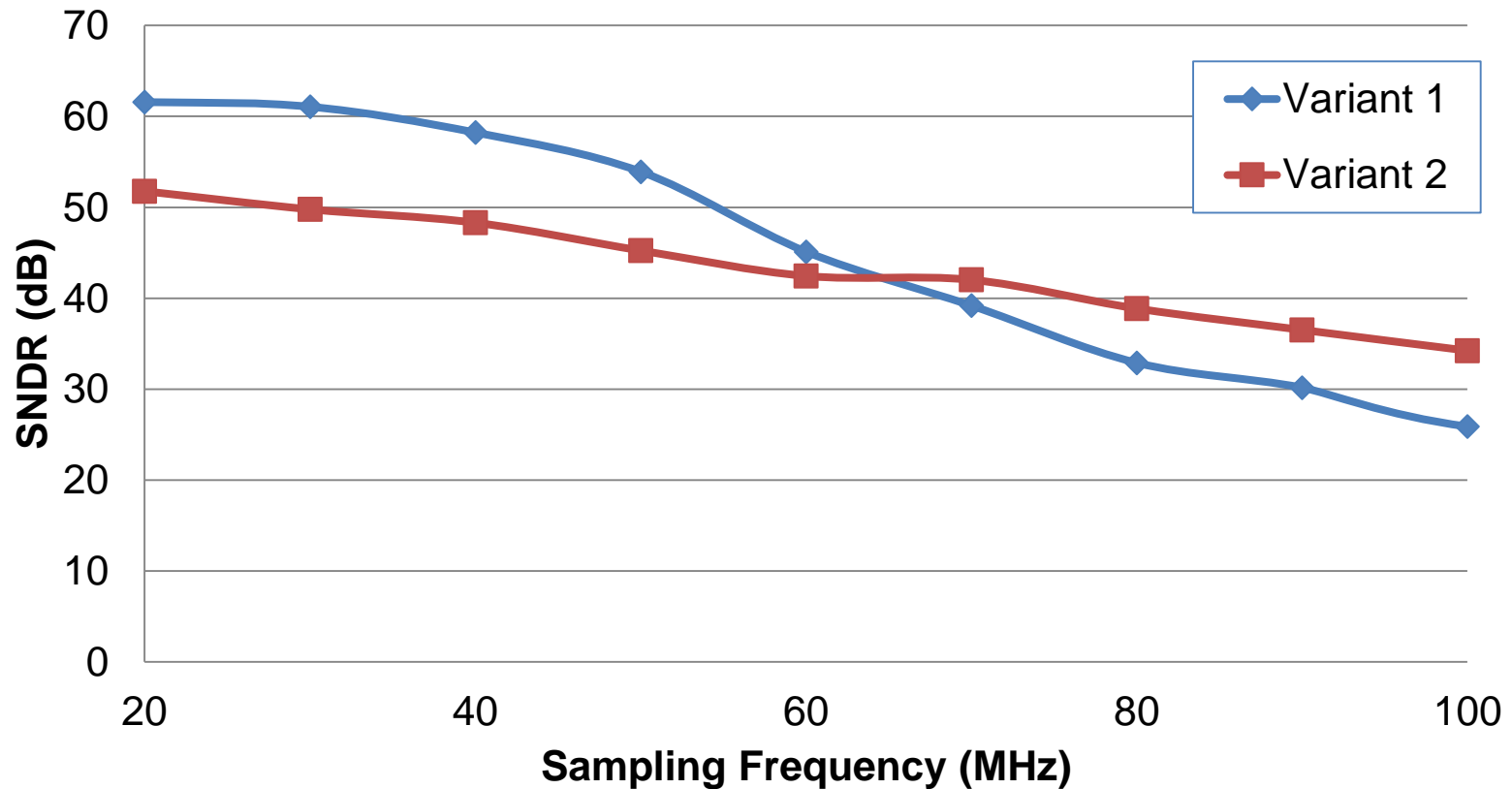


Rail-to-Rail Output Swing

Rail-to-rail output swing test

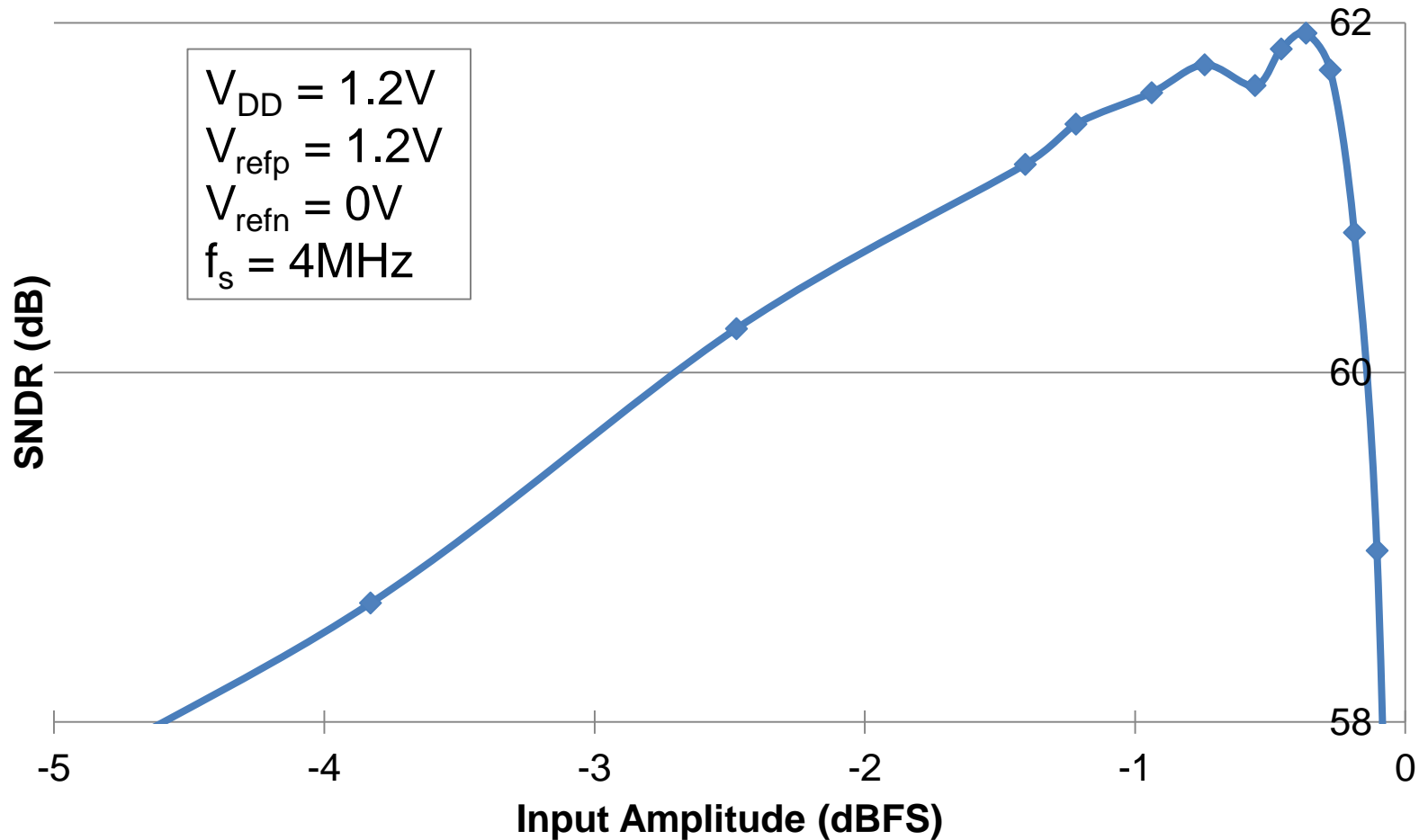

Ring Amp Supply Sensitivity

Ring Amplifier Supply Sensitivity

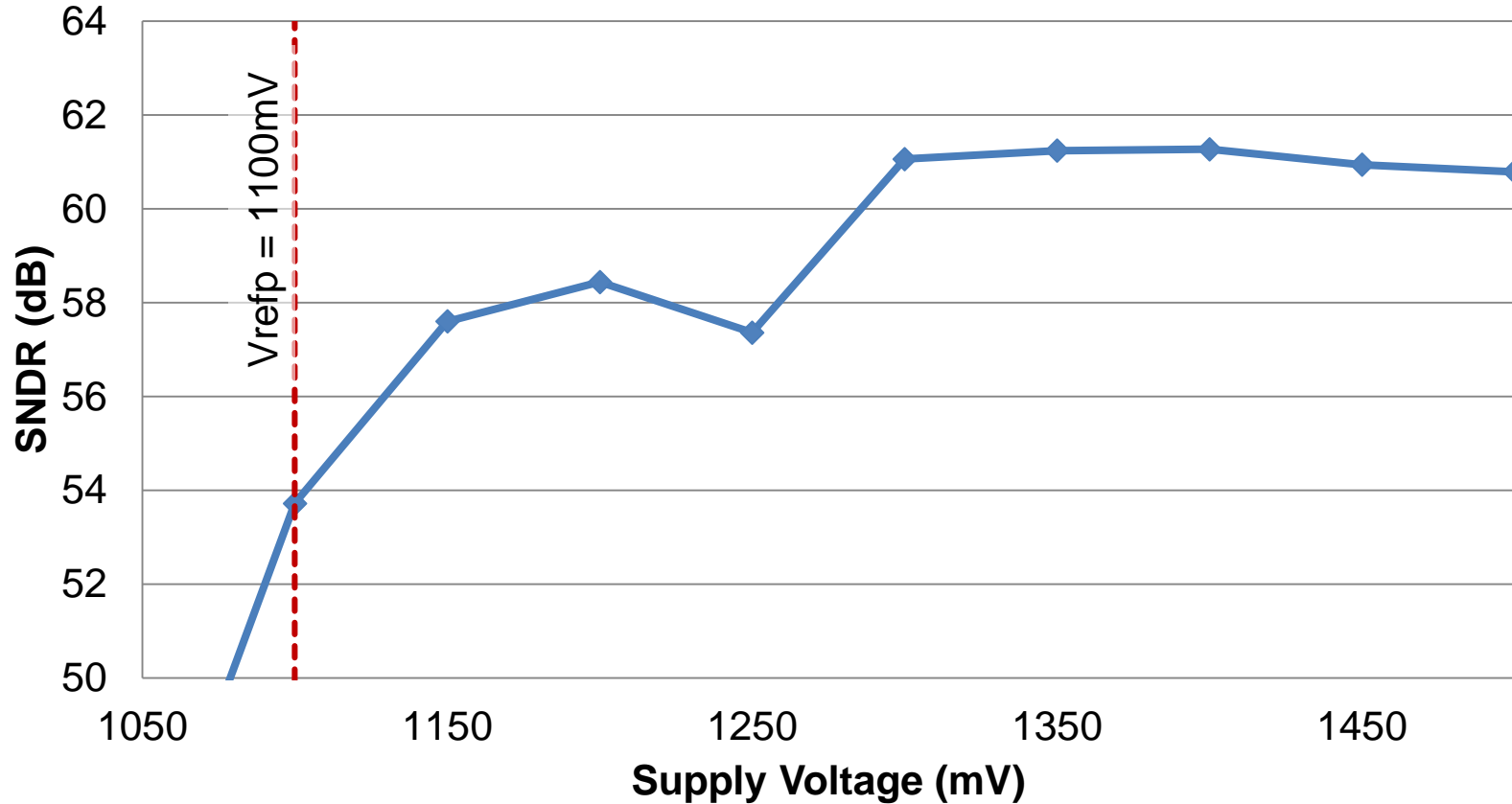

Supply Current vs. Dead-zone

